

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

CSE/CEN 598 Hardware Security & Trust

Trusted Digital System Design: Verilog Fundamentals I

Prof. Michel A. Kinsky & Mishel Paul

1

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Computer System Description

- A system is a set of related components that works as a whole to achieve a goal.
- A system contains:
 - Inputs
 - Behavior
 - Outputs
- Behavior is a function that translates inputs to outputs




2

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Integrated Circuit Based Designs

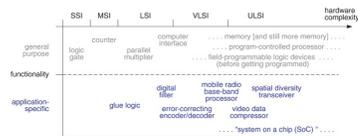- Complex digital integrated circuits (ICs) are manufactured with the advent of Microelectronics Technology
 - The number of components fitted into a standard size IC represents its integration scale, also called density



3

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Digital System Design

- Characteristics of digital systems
 - Synchronous vs. Asynchronous
 - Sequential vs. Combinational
 - Design parameters

4

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Digital Design Flow

Design Stage	Tools
HDL Design (Verilog, VHDL, Bluespec)	Text Editor Emacs, NetEdit, VI
Verification	Mentor - ModelSim SE Synopsys - Leda
Synthesis	Synopsys - Design Compiler
Test Insertion	Synopsys - TetraMax Mentor - Ictacon
Static Timing Anal.	Synopsys - PrimeTime
Place & Route	Cadence - Sencemba/ SOC Encounter Synopsys - Apollo
Clock Tree Insertion	Cadence - ClTree
Timing Extraction	Synopsys - StarRC Cadence - Prol
DRC/ANT Checking	Cadence - Assura, Dracula Mentor - Calibre
LVS	Cadence - Assura, Dracula Mentor - Calibre

5

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Digital Design Flow: FPGA Design

- FPGA-based design as a sub-domain of digital design

6

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

RTL Design Tools


- In this class, we will learn the principles of RTL (register level transfer) coding for synthesis tools through the Verilog hardware description language (HDL) for the design and documentation of out electronic systems.
 - Verilog allows designers to design at various levels of abstraction.
 - It is the most widely used HDL

7

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Programmable Logics

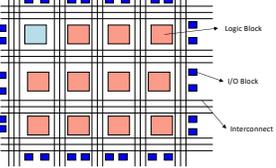- Field Programmable Gate Arrays (more on it later)
 - Each cell in array contains a programmable logic function




The diagram shows a grid of logic blocks (orange squares) connected by interconnects (grey lines). Blue squares represent I/O blocks. Labels with arrows point to a Logic Block, an I/O Block, and an Interconnect.

8

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Programmable Logics

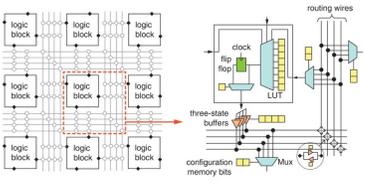- Field Programmable Gate Arrays (more on it later)
 - Array has programmable interconnect between logic functions



The diagram illustrates the internal structure of an FPGA. It shows a grid of logic blocks connected by routing wires. A detailed view of a logic block shows it contains a flip flop, a LUT (Look-Up Table), and three-state buffers. Configuration memory bits are used to control the routing and logic functions. Labels include logic block, routing wires, flip flop, LUT, three-state buffers, configuration memory bits, and Mux.

9

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Verilog Fundamentals

- Data types
- Structural Verilog
- Functional Verilog
 - Gate level
 - Register transfer level
 - High-level behavioral

10

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Primary Verilog data type

- Primary Verilog data type is a bit-vector where bits can take

Value	Meaning
0	Logic zero
1	Logic one
X	Unknown logic value
Z	High impedance, floating

An X bit might be a 0, 1, Z, or in transition. We can set bits to be X in situations where we don't care what the value is. This can help catch bugs and improve synthesis quality

11

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Verilog wire

- The Verilog keyword `wire` is used to denote a standard hardware net

```

wire [15:0] instruction;
wire [15:0] memory_req;
wire [ 7:0] small_net;

```

Absolutely no type safety when connecting nets!

12

STAM Center STRONG, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Verilog bit literals

- Verilog includes ways to specify **bit literals** in various bases

4' b10_11

↑ ↑ ↑

Base format (d,b,o,h)

↑ ↑ ↑

Decimals number representing size in bits

↑ ↑ ↑

Underscores are ignored

- Binary literals
 - 8'b0000_0000
 - 8'b0xx0_1xx1
- Hexadecimal literals
 - 32'h0a34_def1
 - 16'haxxx
- Decimal literals
 - 32'd42

13

STAM Center STRONG, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Verilog module specification

- A Verilog module includes a module name and a port list

Ports must have a direction (or be bidirectional) and a bitwidth

```

module adder( A, B, cout, sum );
input  [3:0] A;
input  [3:0] B;
output cout;
output [3:0] sum;
// HDL modeling of
// adder functionality
endmodule

```

Note the semicolon at the end of the port list!

14

STAM Center STRONG, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Verilog module specification

- A Verilog module includes a module name and a port list

Traditional Verilog-1995 Syntax

```

module adder( A, B, cout, sum );
input  [3:0] A;
input  [3:0] B;
output cout;
output [3:0] sum;

```

ANSI C Style Verilog-2001 Syntax

```

module adder( input [3:0] A,
input [3:0] B,
output cout,
output [3:0] sum );

```

15

STAM Center
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

ASU Engineering
Arizona State University

Module composition

- A module can instantiate other modules creating a module

```

module FA( input a, b, cin
          output cout, sum
);
// HDL modeling of 1 bit
// adder functionality
endmodule

```

16

STAM Center
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

ASU Engineering
Arizona State University

Module composition

```

module adder( input [3:0] A, B,
             output cout,
             output [3:0] S );

wire c0, c1, c2;
FA fa0( ... );
FA fa1( ... );
FA fa2( ... );
FA fa3( ... );
endmodule

```

17

STAM Center
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

ASU Engineering
Arizona State University

Module composition

```

module adder( input [3:0] A, B,
             output cout,
             output [3:0] S );

wire c0, c1, c2;
FA fa0( A[0], B[0], 1'b0, c0, S[0] );
FA fa1( A[1], B[1], c0, c1, S[1] );
FA fa2( A[2], B[2], c1, c2, S[2] );
FA fa3( A[3], B[3], c2, cout, S[3] );
endmodule
          Carry Chain

```

18

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Module composition

- Verilog supports connecting ports by position and by name

Connecting ports by ordered list

```
FA fa0( A[0], B[0], 1'b0, c0, S[0] );
```

Connecting ports by name (compact)

```
FA fa0( .a(A[0]), .b(B[0]),
        .cin(1'b0), .cout(c0), .sum(S[0]) );
```

Connecting ports by name

```
FA fa0
(
  .a (A[0]),
  .b (B[0]),
  .cin (1'b0),
  .cout (c0),
  .sum (S[0])
);
```

For all but the smallest modules, connecting ports by name yields clearer and less buggy code.

19

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Functional Verilog

- Functional Verilog can roughly be divided into three abstraction levels

20

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Gate-level Verilog

```
module mux4( input a, b, c, d, input [1:0] sel, output out );
  wire [1:0] sel_b;
  not not0( sel_b[0], sel[0] );
  not not1( sel_b[1], sel[1] );
  wire n0, n1, n2, n3;
  and and0( n0, c, sel[1] );
  and and1( n1, a, sel_b[1] );
  and and2( n2, d, sel[1] );
  and and3( n3, b, sel_b[1] );
  wire x0, x1;
  nor nor0( x0, n0, n1 );
  nor nor1( x1, n2, n3 );
  wire y0, y1;
  or or0( y0, x0, sel[0] );
  or or1( y1, x1, sel_b[0] );
  nand nand0( out, y0, y1 );
endmodule
```

21

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Continuous Assignments

- Continuous assignment statements assign one net to another or to a literal

Explicit continuous assignment

```
wire [15:0] netA;
wire [15:0] netB;

assign netA = 16'h3333;
assign netB = netA;
```

Implicit continuous assignment

```
wire [15:0] netA = 16'h3333;
wire [15:0] netB = netA;
```

22

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Continuous Assignments

- Using continuous assignments to implement an RTL four input multiplexer

```
module mux4( input a, b, c, d
            input [1:0] sel,
            output out );

    wire out, t0, t1;

    assign t0 = ~( sel[1] & c ) | ( ~sel[1] & a );
    assign t1 = ~( sel[1] & d ) | ( ~sel[1] & b );
    assign out = ~( t0 | sel[0] ) & ( t1 | ~sel[0] );

endmodule
```

The order of these continuous assignment statements does not matter. They essentially happen in parallel!

23

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Other Verilog Operators

- Verilog RTL includes many operators in addition to basic boolean logic

```
// Four input multiplexer
module mux4( input a, b, c, d
            input [1:0] sel,
            output out );

    assign out = ( sel == 0 ) ? a :
                ( sel == 1 ) ? b :
                ( sel == 2 ) ? c :
                ( sel == 3 ) ? d : 1'bx;

endmodule
```

If input is undefined, we want to propagate that information

```
// Simple four bit adder
module adder( input [3:0] op1, op2,
             output [3:0] sum );

    assign sum = op1 + op2;

endmodule
```

24

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future Starts Here
Arizona State University

Verilog RTL operators

Arithmetic	+ - * / % **	Reduction	& ~& ~ ^ ^~
Logical	! &&	Shift	>> << >>> <<<
Relational	> < >= <=	Concatenation	{ }
Equality	== != === !==	Conditional	?:
Bitwise	~ & ^ ~		

```

wire [ 3:0] net1 = 4'b00xx;
wire [ 3:0] net2 = 4'b1110;
wire [11:0] net3 = { 4'b0, net1, net2 };
wire equal = ( net3 == 12'b0000_1110_00xx );
    
```

Avoid (/ % **) since the usually synthesize poorly

25

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future Starts Here
Arizona State University

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input a, b, c, d
            input [1:0] sel,
            output out );
    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    end
endmodule
    
```

The always block is reevaluated whenever a signal in its sensitivity list changes

26

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future Starts Here
Arizona State University

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input a, b, c, d
            input [1:0] sel,
            output out );
    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    end
endmodule
    
```

The order of these procedural assignment statements does matter. They essentially happen in sequentially!

27

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future Starts Here
Arizona State University

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
  reg out, t0, t1;
  always @( a or b or c or d or sel )
  begin
    t0 = ~( sel[1] & c ) | ( ~sel[1] & a );
    t1 = ~( sel[1] & d ) | ( ~sel[1] & b );
    out = ~( t0 | sel[0] ) & ( t1 | ~sel[0] );
  end
endmodule
    
```

LHS of procedural assignments must be declared as a reg type. Verilog reg is not necessarily a hardware register!

28

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future Starts Here
Arizona State University

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
  reg out, t0, t1;
  always @( a or b or c or X or sel )
  begin
    t0 = ~( sel[1] & c ) | ( ~sel[1] & a );
    t1 = ~( sel[1] & d ) | ( ~sel[1] & b );
    out = ~( t0 | sel[0] ) & ( t1 | ~sel[0] );
  end
endmodule
    
```

What happens if we accidentally forget a signal on the sensitivity list?

29

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future Starts Here
Arizona State University

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
  reg out, t0, t1;
  always @( a or b or c or d or sel )
  begin
    t0 = ~( sel[1] & c ) | ( ~sel[1] & a );
    t1 = ~( sel[1] & d ) | ( ~sel[1] & b );
    out = ~( t0 | sel[0] ) & ( t1 | ~sel[0] );
  end
endmodule
    
```

Verilog-2001 provides special syntax to automatically create a sensitivity list for all signals read in the always block

30

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Assignments

- Continuous and procedural assignment statements are very different

Continuous assignments are for naming and thus we cannot have multiple assignments for the same wire

```

wire out, t0, t1;
assign t0 = ~(sel[1] & c) | (~sel[1] & a);
assign t1 = ~(sel[1] & d) | (~sel[1] & b);
assign out = ~(t0 | sel[0]) & (t1 | ~sel[0]);
    
```

Procedural assignments hold a value semantically, but it is important to distinguish this from hardware state

```

reg out, t0, t1, temp;
always @( * )
begin
temp = ~(sel[1] & c) | (~sel[1] & a);
t0 = temp;
temp = ~(sel[1] & d) | (~sel[1] & b);
t1 = temp;
out = ~(t0 | sel[0]) & (t1 | ~sel[0]);
end
    
```

31

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Always Blocks

- Always blocks can contain more advanced control constructs

```

module mux4( input a, b, c, d
            input [1:0] sel,
            output out );
    reg out;
    always @( * )
    begin
        if ( sel == 2'd0 )
            out = a;
        else if ( sel == 2'd1 )
            out = b;
        else if ( sel == 2'd2 )
            out = c;
        else if ( sel == 2'd3 )
            out = d;
        else
            out = 1'bx;
    end
endmodule
    
```

```

module mux4( input a, b, c, d
            input [1:0] sel,
            output out );
    reg out;
    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            2'd3 : out = d;
            default : out = 1'bx;
        endcase
    end
endmodule
    
```

32

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Case Statements

- What happens if the case statement is not complete?

```

module mux3( input a, b, c
            input [1:0] sel,
            output out );
    reg out;
    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
        endcase
    end
endmodule
    
```

If sel = 3, mux will output the previous value. What have we created?

33

STAM Center STRONG, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Case Statements

- What happens if the case statement is not complete?

```

module mux3( input a, b, c,
             input [1:0] sel,
             output out );
  reg out;
  always @( * )
  begin
    case ( sel )
      2'd0 : out = a;
      2'd1 : out = b;
      2'd2 : out = c;
      default : out = 1'bx;
    endcase
  end
endmodule

```

We can prevent creating state with a default statement

34

STAM Center STRONG, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Latches and Flip-flops

```

module latch
(
  input clk,
  input d,
  output reg q
);
  always @( clk )
  begin
    if ( clk )
      d = q;
  end
endmodule

module flipflop
(
  input clk,
  input d,
  output q
);
  always @( posedge clk )
  begin
    d = q;
  end
endmodule

```

Edge-triggered always block

35

STAM Center STRONG, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg A_out, B_out, C_out;

always @( posedge clk )
  A_out = A_in;

assign B_in = A_out + 1;

always @( posedge clk )
  B_out = B_in;

assign C_in = B_out + 1;

always @( posedge clk )
  C_out = C_in;

```

36

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;

```

A

1

B

2

C

Active Event Queue



On clock edge all those events which are sensitive to the clock are added to the active event queue in any order!

37

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;

```

A

1

B

2

C

Active Event Queue



38

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;

```

A


1

B

2

C

Active Event Queue

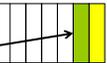

39

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;
    
```

Active Event Queue

40

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;
    
```

Active Event Queue

A evaluates and as a consequence 1 is added to the event queue

41

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;
    
```

Active Event Queue

Event queue is emptied before we go to next clock cycle

42

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;
    
```

A

1

B

2

C

Active Event Queue

Event queue is emptied before we go to next clock cycle

43

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;
    
```

A

1

B

2

C

44

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Non-Blocking Assignments

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out <= A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out <= B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out <= C_in;
    
```

Non-blocking procedural assignments add an extra event queue

A

1

B

2

C

Active Event Queue

Non-Blocking Queue

45

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Non-Blocking Assignments

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out <= A_in;
assign B_in = A_out + 1;
always @(posedge clk)
  B_out <= B_in;
assign C_in = B_out + 1;
always @(posedge clk)
  C_out <= C_in;
    
```

Non-blocking procedural assignments add an extra event queue

A

1

B

2

C

46

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Non-Blocking Assignments

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
begin
  A_out <= A_in;
  B_out <= B_in;
  C_out <= C_in;
end

assign B_in = A_out + 1;
assign C_in = B_out + 1;
    
```

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
begin
  C_out <= C_in;
  B_out <= B_in;
  A_out <= A_in;
end

assign B_in = A_out + 1;
assign C_in = B_out + 1;
    
```

The order of non-blocking assignments does not matter!

47

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Common Patterns

- Common patterns for latch and flip-flop inference

```

always @( clk )
begin
  if ( clk )
    D <= Q;
end
    
```

```

always @(posedge clk)
begin
  D <= Q;
end
    
```

```

always @(posedge clk)
begin
  if ( enable )
    D <= Q;
end
    
```

→

→

→

48

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Blocking vs. Non-blocking

- Guidelines for using blocking and non-blocking assignment statements
 - Flip-flops should use non-blocking
 - Latches should use non-blocking
 - Combinational logic should use blocking
 - Do not mix combinational and sequential logic in the same always block
 - Do not assign to the same variable from more than one always block

49

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

Behavioral Verilog Usage

- Behavioral Verilog is used to model the abstract function of a hardware module
 - Characterized by heavy use of sequential blocking statements in large always blocks
 - Many constructs are not synthesizable but can be useful for behavioral modeling
 - Data dependent for and while loops
 - Additional behavioral datatypes : `integer`, `real`
 - Magic initialization blocks : `initial`
 - Magic delay statements: `#<delay>`

50

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

High-level Behavior

- Verilog can be used to model the high-level behavior of a hardware block

```

module factorial( input [ 7:0] in, output reg
[15:0] out );
  integer num_calls;
  initial num_calls = 0;
  integer multiplier;
  integer result;

  always @(*)
  begin
    multiplier = in;
    result = 1;
    while ( multiplier > 0 )
    begin
      result = result * multiplier;
      multiplier = multiplier - 1;
    end

    out = result;
    num_calls = num_calls + 1;
  end
endmodule

```

Annotations in the slide:

- Initial statement: points to `initial num_calls = 0;`
- Variables of type integer: points to `integer multiplier;` and `integer result;`
- Data dependent while loop: points to the `while` loop

51

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

Delay Statements

- Delay statements should only be used in test

```

module mux4
(
  input a,
  input b,
  input c,
  input d,
  input [1:0] sel,
  output out
);
  wire #10 t0 = ~( sel[1] & c ) | (~sel[1] & a );
  wire #10 t1 = ~( sel[1] & d ) | (~sel[1] & b );
  wire #10 out = ~( t0 | sel[0] ) & (t1 | ~sel[0]);
endmodule
    
```

Although this will add a delay for simulation, these are ignored in synthesis

52

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University


Synthesizable Blocks

- Even synthesizable blocks can be more behavioral

```

module ALU
(
  input [31:0] in0,
  input [31:0] in1,
  input [1:0] fn,
  output [31:0] out
);
  assign out
    = { fn == 2'd0 } ? ( in0 + in1 )
      : { fn == 2'd1 } ? ( in0 - in1 )
        : { fn == 2'd9 } ? ( in1 >> in0 )
          : { fn == 2'd10 } ? ( in1 >>> in0 )
            : 32'bX;
endmodule
    
```

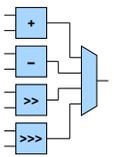Although this module is synthesizable, it is unlikely to produce the desired hardware



53

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** The Future School of Arizona State University

System Testing

```

reg [ 1023:0 ] exe_filename;

initial
begin
  // This turns on VCD (plus) output
  $vcdpluson(0);

  // This gets the program to load into memory from the command line
  if ( $exists($plusargs("exe=")) )
    $readmemh( exe_filename, mem.m );
  else
  begin
    $display( "ERROR: No executable specified! (use exe=<filename>)" );
    $finish;
  end

  // Strobe reset
  #0 reset = 1;
  #30 reset = 0;

end
    
```

54

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** THE FUTURE SCHOOLS OF ARIZONA STATE UNIVERSITY

Which abstraction is the right one?

```

graph TD
    A[High-Level Behavioral] --> B[Register Transfer Level]
    B --> C[Gate Level]
  
```

- Designers usually use a mix of all three
 - Early in the design process they might use mostly behavioral models.
 - As the design is refined, the behavioral models begin to be replaced by dataflow models.
 - Finally, the designers use automatic tools to synthesize a low-level gate-level model

55

STAM Center SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** THE FUTURE SCHOOLS OF ARIZONA STATE UNIVERSITY

Take away points

- Structural Verilog enables us to describe a hardware schematic textually
- Verilog can model hardware at three levels of abstraction
 - Gate level, register transfer level, and behavioral
- Understanding the Verilog execution semantics is critical for understanding blocking + non-blocking assignments
- Designers must have the hardware they are trying to create in mind when they write their Verilog

56
