

CSE/CEN 598


Hardware Security & Trust

Trusted Digital System Design:
Verilog Fundamentals I

Prof. Michel A. Kinsy & Mishel Paul

Computer System Description

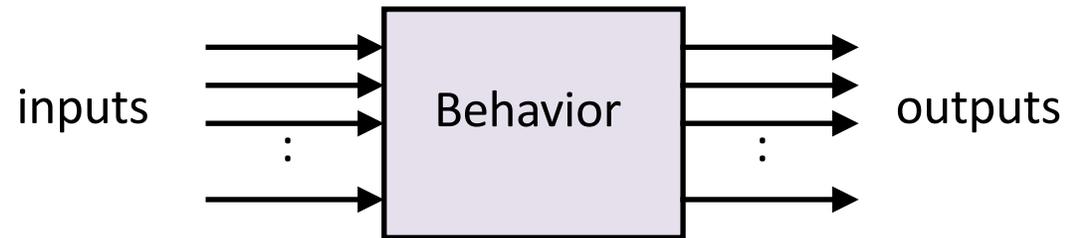
- A system is a set of related components that works as a whole to achieve a goal.
- A system contains:
 - Inputs
 - Behavior
 - Outputs




- Behavior is a function that translates inputs to outputs

Integrated Circuit Based Designs

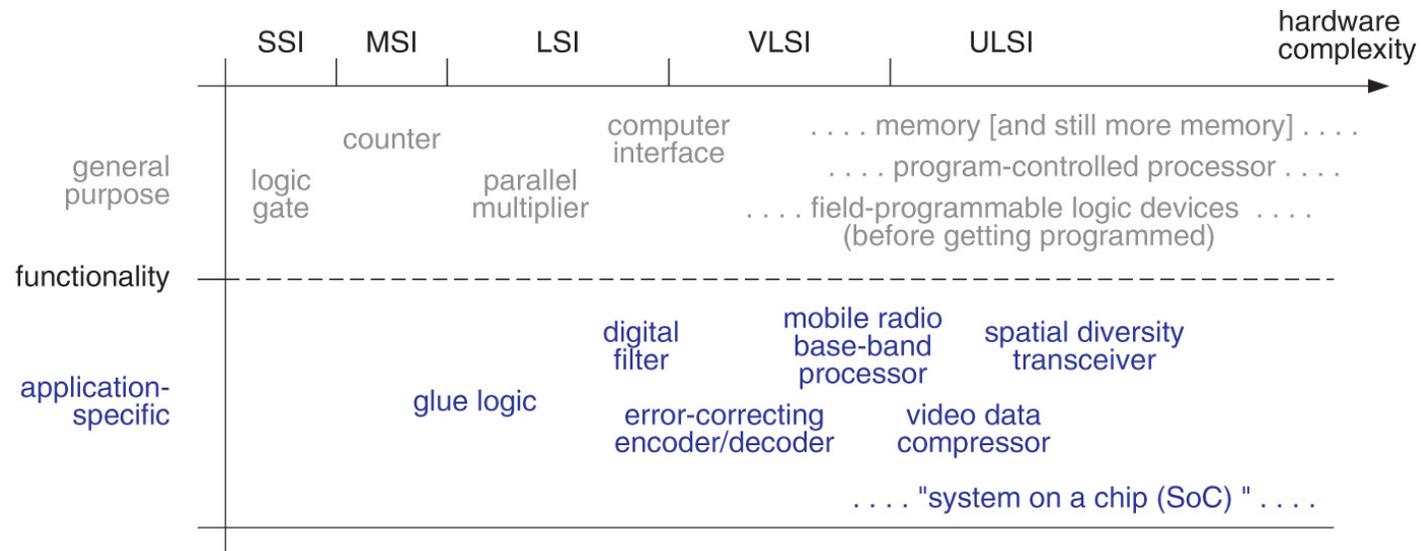- Complex digital integrated circuits (ICs) are manufactured with the advent of Microelectronics Technology
 - The number of components fitted into a standard size IC represents its integration scale, also called density




Digital System Design

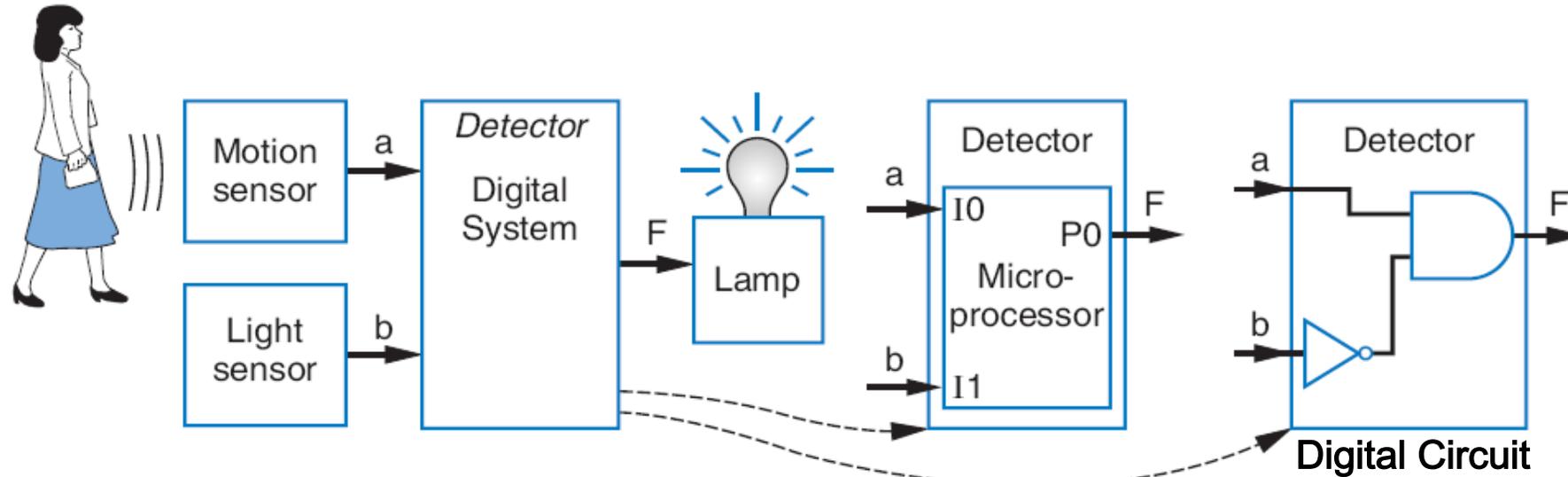

- Characteristics of digital systems
 - Synchronous vs. Asynchronous
 - Sequential vs. Combinational
 - Design parameters


Digital Design Flow

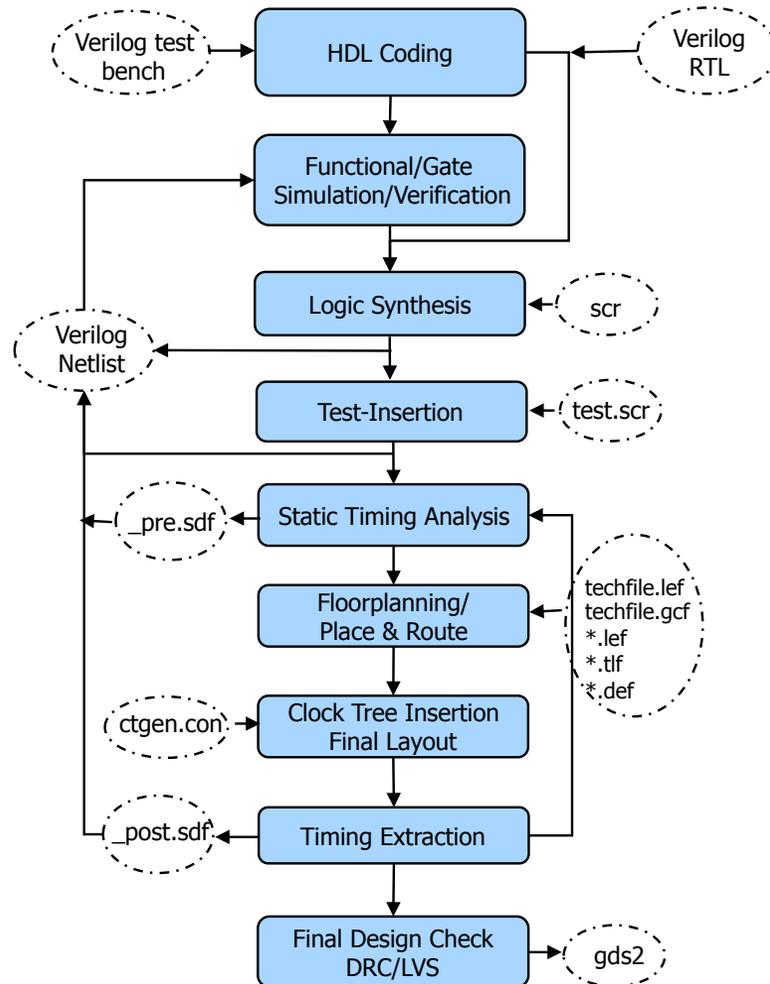

Design Stage	Tools
HDL Design (Verilog, VHDL, Bluespec)	Text Editor Emacs, Nedit, Vi
Verification	Mentor - Modelsim SE Synopsys - Leda
Synthesis	Synopsys - Design Compiler
Test Insertion	Synopsys - TetraMax Mentor - Fastscan
Static Timing Anal.	Synopsys - Primetime
Place & Route	Cadence - Sensible/ SOC Encounter Synopsys - Apollo
Clock Tree Insertion	Cadence - CTgen
Timing Extraction	Synopsys - StarRXT Cadence - Pearl
DRC/ANT Checking	Cadence - Assura, Dracula Mentor - Callibre
LVS	Cadence - Assura, Dracula Mentor - Callibre

Digital Design Flow: FPGA Design

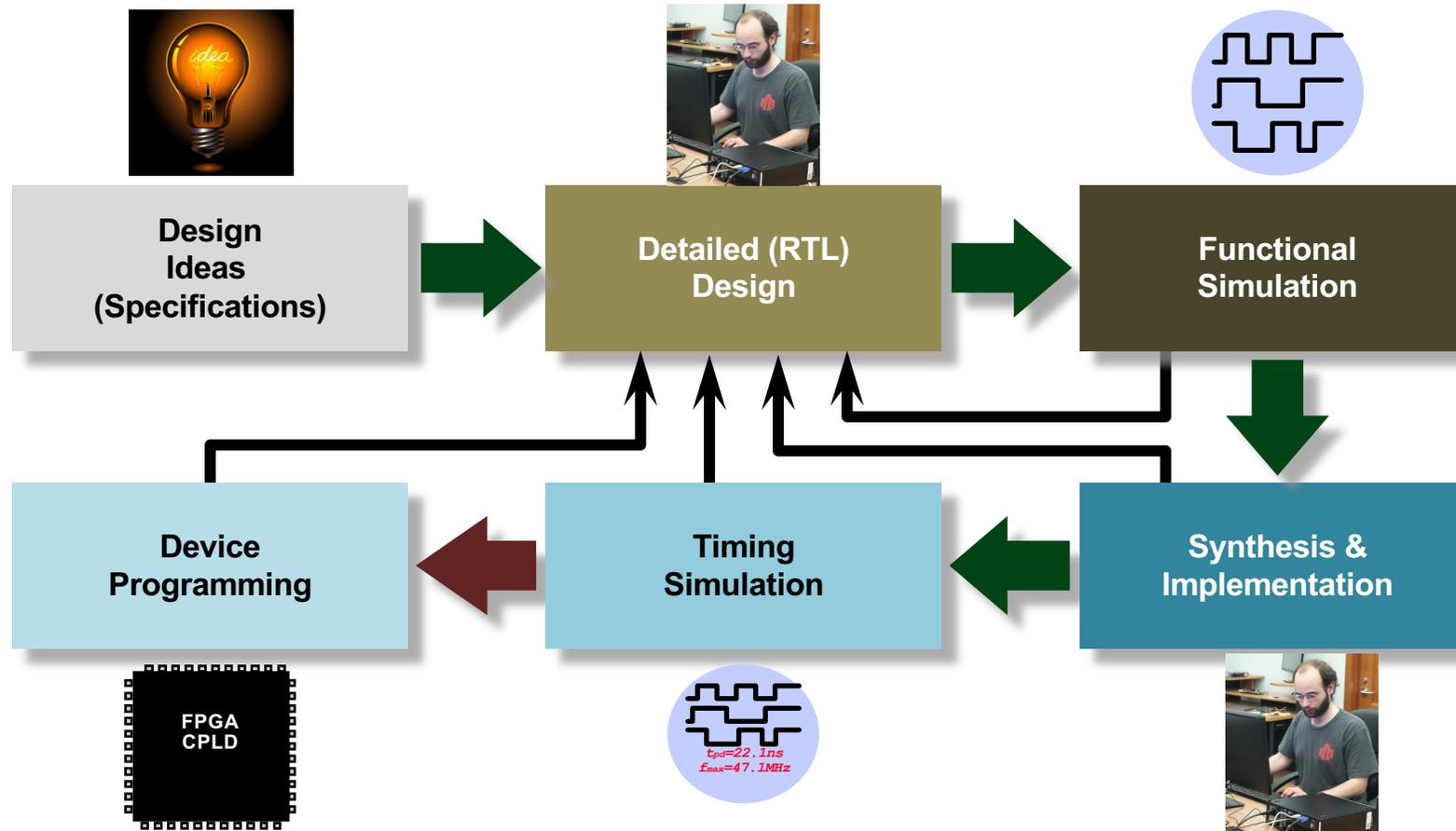- FPGA-based design as a sub-domain of digital design




RTL Design Tools

- In this class, we will learn the principles of RTL (register level transfer) coding for synthesis tools through the Verilog hardware description language (HDL) for the design and documentation of out electronic systems.
 - Verilog allows designers to design at various levels of abstraction.
 - It is the most widely used HDL


Programmable Logics

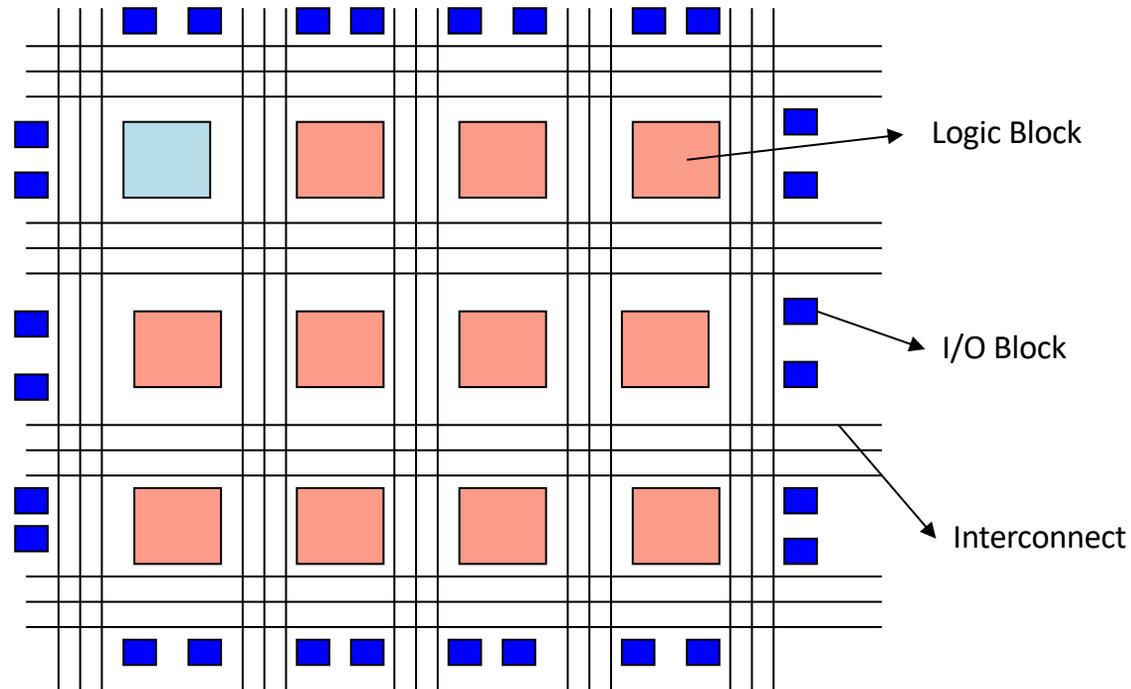- Field Programmable Gate Arrays (more on it later)
 - Each cell in array contains a programmable logic function



Programmable Logics

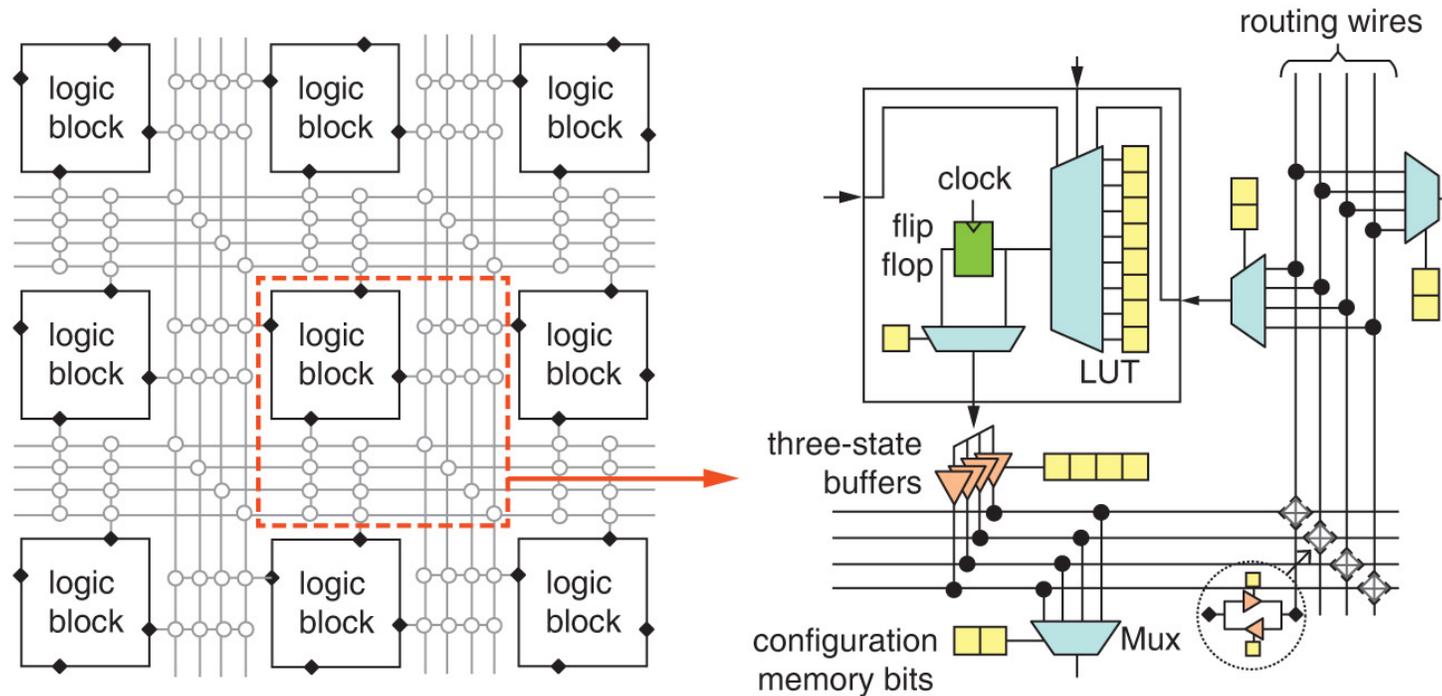- Field Programmable Gate Arrays (more on it later)
 - Array has programmable interconnect between logic functions




Verilog Fundamentals

- Data types
- Structural Verilog
- Functional Verilog
 - Gate level
 - Register transfer level
 - High-level behavioral

Primary Verilog data type

- Primary Verilog data type is a bit-vector where bits can take

Value	Meaning
0	Logic zero
1	Logic one
X	Unknown logic value
Z	High impedance, floating

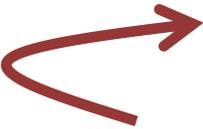



An X bit might be a 0, 1, Z, or in transition. We can set bits to be X in situations where we don't care what the value is. This can help catch bugs and improve synthesis quality

Verilog wire

- The Verilog keyword **wire** is used to denote a standard hardware net


```
wire [15:0] instruction;  
wire [15:0] memory_req;  
wire [ 7:0] small_net;
```

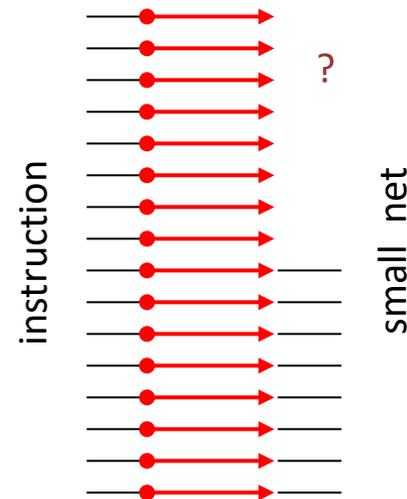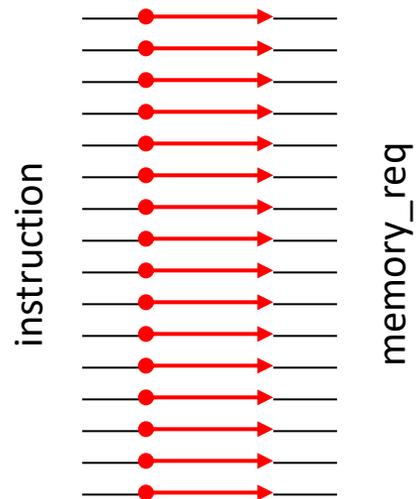Absolutely no type safety
when connecting nets!



Verilog bit literals

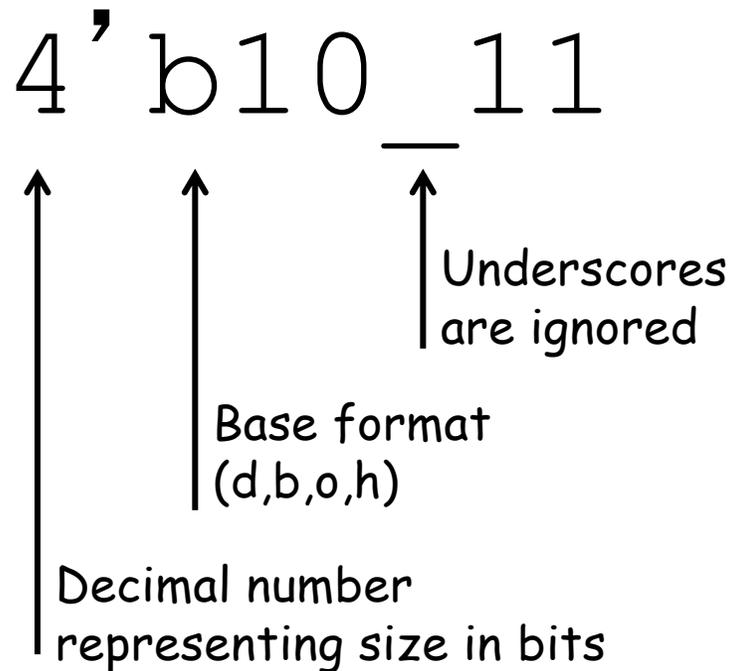
- Verilog includes ways to specify **bit literals** in various bases



- Binary literals
 - 8'b0000_0000
 - 8'b0xx0_1xx1
- Hexadecimal literals
 - 32'h0a34_def1
 - 16'haxxx
- Decimal literals
 - 32'd42

Verilog module specification

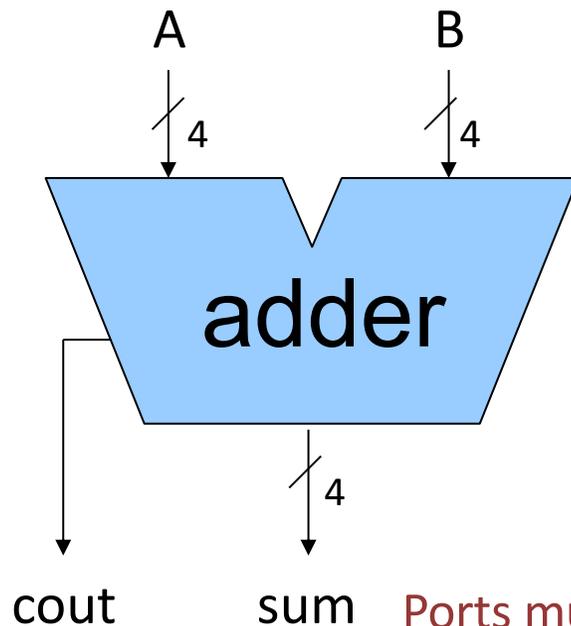- A Verilog module includes a module name and a port list




```
module adder( A, B, cout, sum );  
    input  [3:0] A;  
    input  [3:0] B;  
    output          cout;  
    output [3:0] sum;  
  
    // HDL modeling of  
    // adder functionality  
  
endmodule
```

Ports must have a direction (or be bidirectional) and a bitwidth

Note the semicolon at the end of the port list!

Verilog module specification

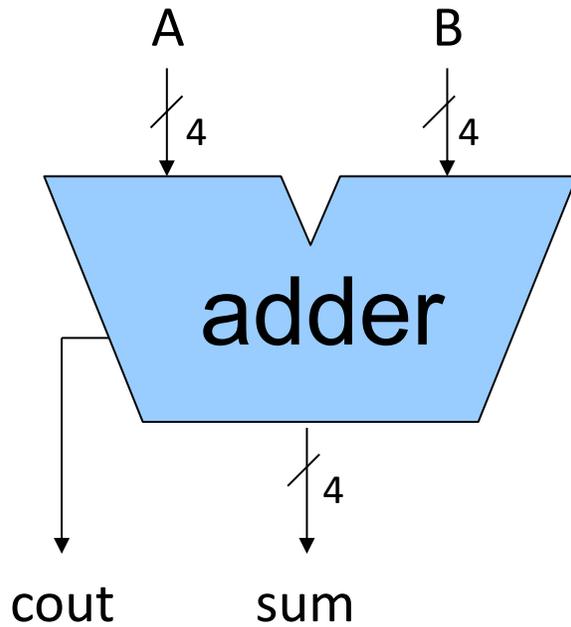- A Verilog module includes a module name and a port list



Traditional Verilog-1995 Syntax


```
module adder( A, B, cout, sum );  
  input  [3:0] A;  
  input  [3:0] B;  
  output          cout;  
  output [3:0] sum;
```

ANSI C Style Verilog-2001 Syntax

```
module adder( input  [3:0] A,  
             input  [3:0] B,  
             output          cout,  
             output [3:0] sum );
```

Module composition

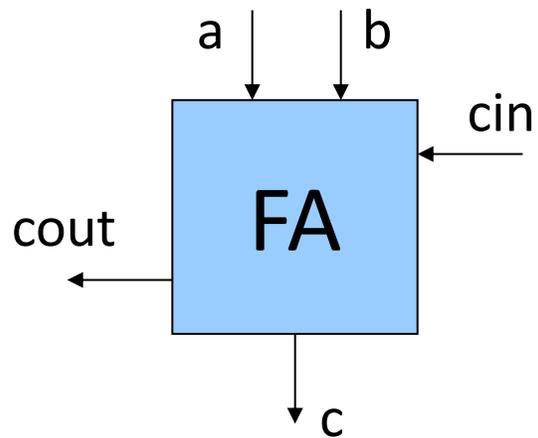- A module can instantiate other modules creating a module




```
module FA( input  a, b, cin
           output cout, sum
);

    // HDL modeling of 1 bit
    // adder functionality

endmodule
```

Module composition

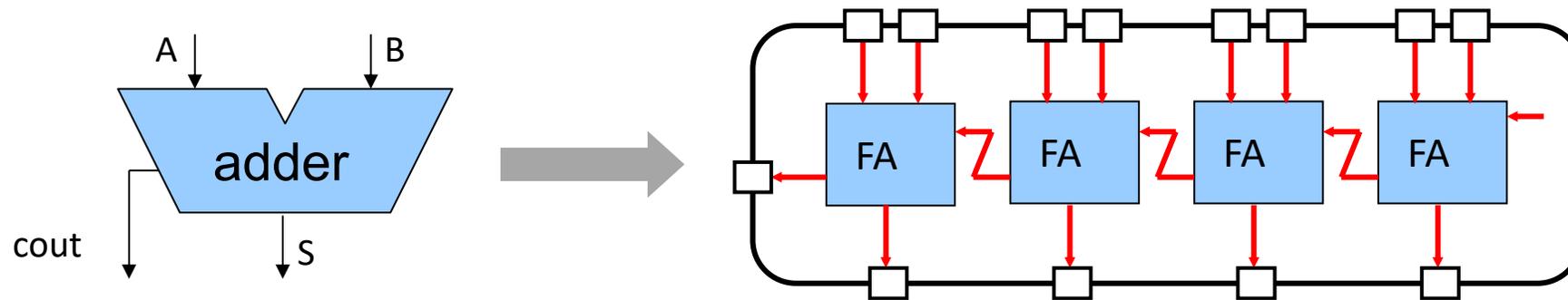

```


module adder( input  [3:0] A, B,
              output   cout,
              output  [3:0] S );

  wire c0, c1, c2;
  FA fa0( ... );
  FA fa1( ... );
  FA fa2( ... );
  FA fa3( ... );

endmodule

```

Module composition

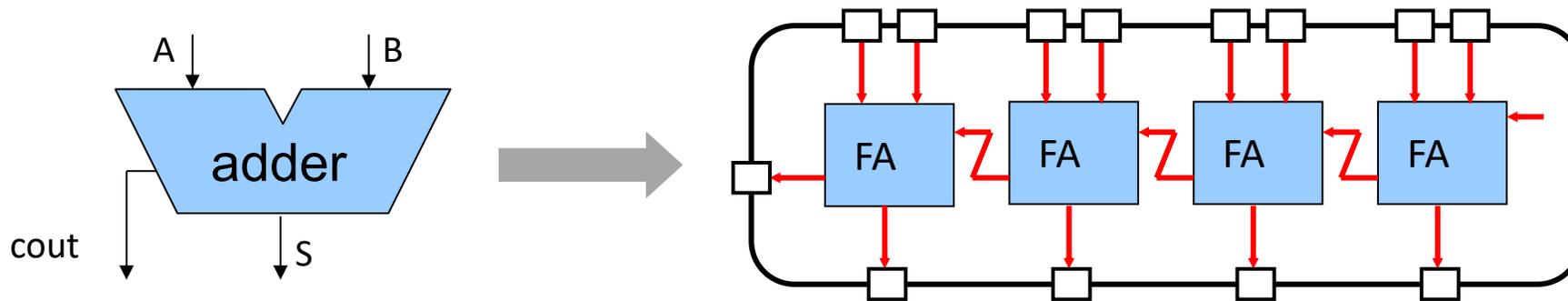

```

module adder( input  [3:0] A, B,
              output   cout,
              output  [3:0] S );

  wire c0, c1, c2;
  FA fa0( A[0], B[0], 1'b0, c0, S[0] );
  FA fa1( A[1], B[1], c0, c1, S[1] );
  FA fa2( A[2], B[2], c1, c2, S[2] );
  FA fa3( A[3], B[3], c2, cout, S[3] );

endmodule

```

Carry Chain

Module composition

- Verilog supports connecting ports by position and by name

Connecting ports by ordered list

```
FA fa0( A[0], B[0], 1'b0, c0, S[0] );
```

Connecting ports by name (compact)

```
FA fa0( .a(A[0]), .b(B[0]),  
        .cin(1'b0), .cout(c0), .sum(S[0]) );
```


Connecting ports by name

```
FA fa0  
(  
  .a    (A[0]),  
  .b    (B[0]),  
  .cin  (1'b0),  
  .cout (c0),  
  .sum  (S[0])  
);
```

For all but the smallest modules,
connecting ports by name yields clearer
and less buggy code.

Functional Verilog

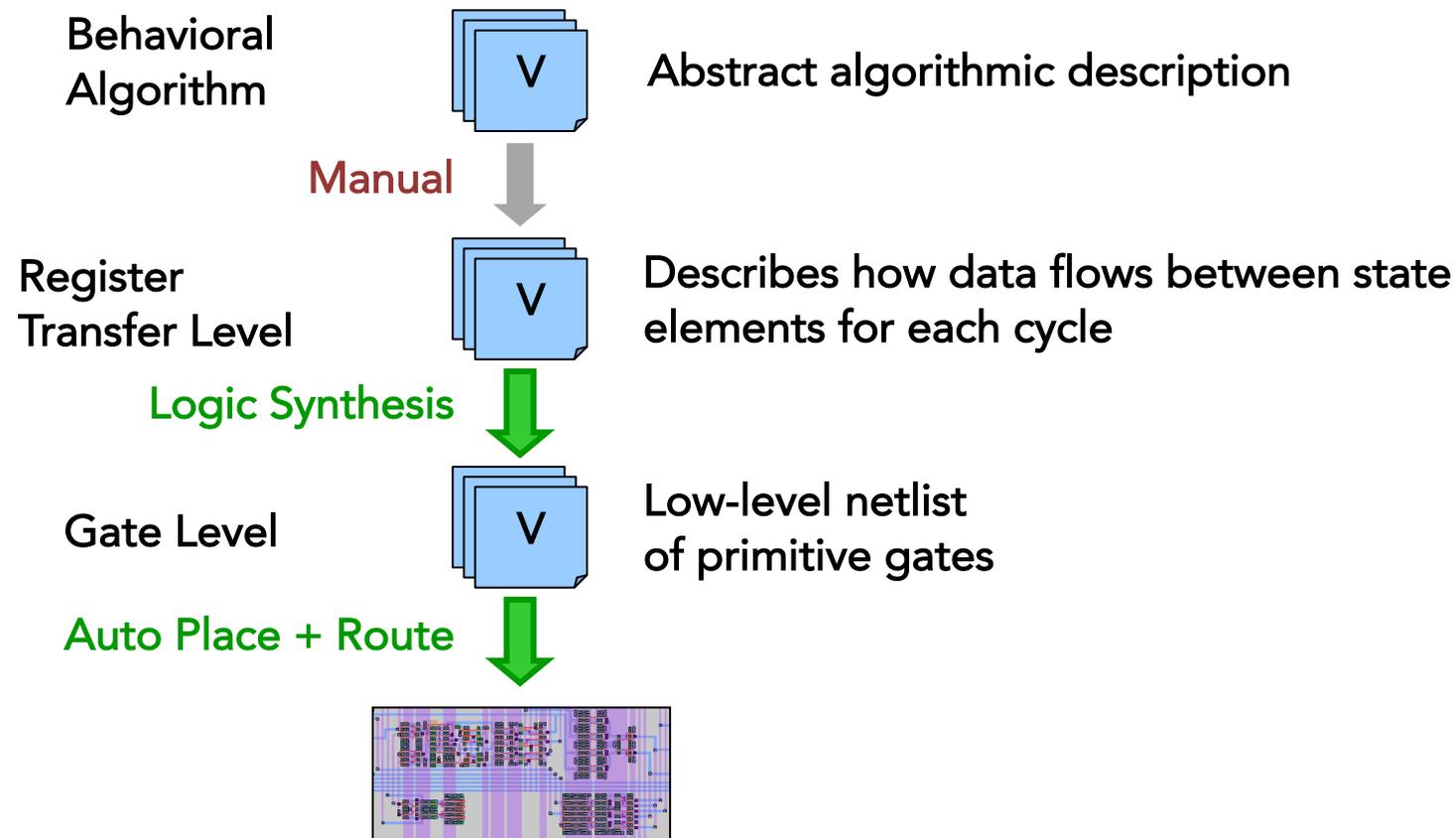- Functional Verilog can roughly be divided into three abstraction levels



Gate-level Verilog

```

module mux4( input  a, b, c, d, input [1:0] sel, output out );

  wire [1:0] sel_b;
  not not0( sel_b[0], sel[0] );
  not not1( sel_b[1], sel[1] );


  wire n0, n1, n2, n3;
  and and0( n0, c, sel[1] );
  and and1( n1, a, sel_b[1] );
  and and2( n2, d, sel[1] );
  and and3( n3, b, sel_b[1] );

  wire x0, x1;
  nor nor0( x0, n0, n1 );
  nor nor1( x1, n2, n3 );

  wire y0, y1;
  or or0( y0, x0, sel[0] );
  or or1( y1, x1, sel_b[0] );
  nand nand0( out, y0, y1 );

endmodule

```

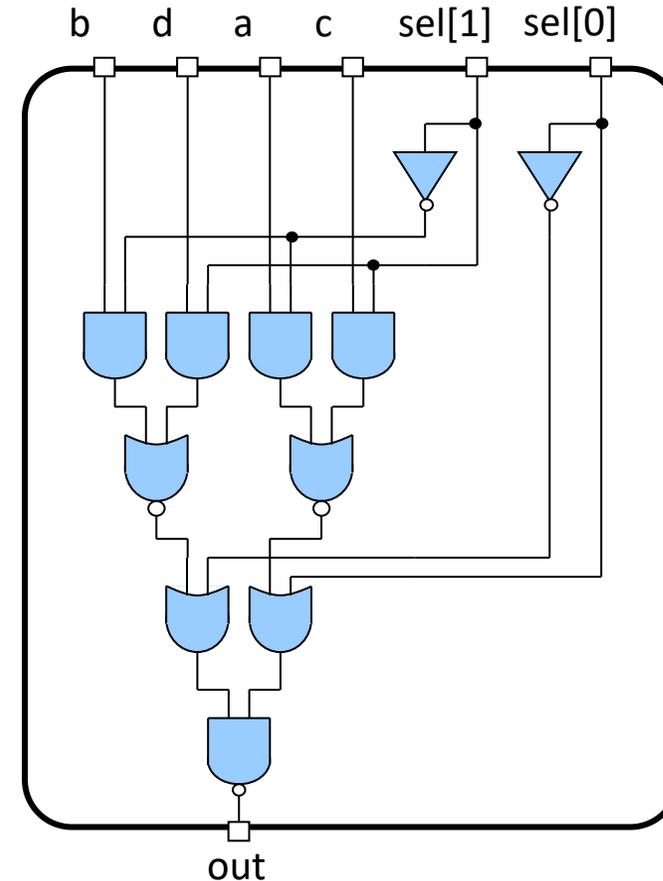

Continuous Assignments

- Continuous assignment statements assign one net to another or to a literal

Explicit continuous assignment

```
wire [15:0] netA;  
wire [15:0] netB;
```

```
assign netA = 16'h3333;  
assign netB = netA;
```

Implicit continuous assignment

```
wire [15:0] netA = 16'h3333;  
wire [15:0] netB = netA;
```

Continuous Assignments

- Using continuous assignments to implement an RTL four input multiplexer

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    wire out, t0, t1;

    assign t0 = ~( (sel[1] & c) | (~sel[1] & a) );
    assign t1 = ~( (sel[1] & d) | (~sel[1] & b) );
    assign out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );

endmodule
```

The order of these continuous assignment statements does not matter. They essentially happen in parallel!

Other Verilog Operators

- Verilog RTL includes many operators in addition to basic boolean logic

```
// Four input multiplexer
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    assign out = ( sel == 0 ) ? a :
                 ( sel == 1 ) ? b :
                 ( sel == 2 ) ? c :
                 ( sel == 3 ) ? d : 1'bx;
```

```
Endmodule
// Simple four bit adder
module adder( input  [3:0] op1, op2,
              output [3:0] sum );

    assign sum = op1 + op2;

endmodule
```

If input is undefined,
we want to propagate
that information

Verilog RTL operators

Arithmetic	+ - * / % **	Reduction	& ~& ~ ^ ^~
Logical	! &&	Shift	>> << >>> <<<
Relational	> < >= <=	Concatenation	{ }
Equality	== != === !===	Conditional	?:
Bitwise	~ & ^ ^~		

```
wire [ 3:0] net1 = 4'b00xx;
wire [ 3:0] net2 = 4'b1110;
wire [11:0] net3 = { 4'b0, net1, net2 };
wire equal = ( net3 === 12'b0000_1110_00xx );
```

Avoid (/ % **) since they usually synthesize poorly

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    end
endmodule
```



The always block is reevaluated whenever a signal in its sensitivity list changes

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    end
endmodule
```

The order of these procedural assignment statements does matter.

They essentially happen in sequentially!

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    end
endmodule

```

LHS of procedural assignments must be declared as a reg type. Verilog reg is not necessarily a hardware register!

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    end
endmodule

```

What happens if we accidentally forget a signal on the sensitivity list?

Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( (sel[1] & c) | (~sel[1] & a) );
        t1 = ~( (sel[1] & d) | (~sel[1] & b) );
        out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
    end
endmodule
```

Verilog-2001 provides special syntax to automatically create a sensitivity list for all signals read in the always block

Assignments

- Continuous and procedural assignment statements are very different

Continuous assignments are for naming and thus we cannot have multiple assignments for the same wire

```
wire out, t0, t1;  
assign t0 = ~( (sel[1] & c) | (~sel[1] & a) );  
assign t1 = ~( (sel[1] & d) | (~sel[1] & b) );  
assign out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
```

Procedural assignments hold a value semantically, but it is important to distinguish this from hardware state

```
reg out, t0, t1, temp;  
always @( * )  
begin  
    temp = ~( (sel[1] & c) | (~sel[1] & a) );  
    t0 = temp;  
    temp = ~( (sel[1] & d) | (~sel[1] & b) );  
    t1 = temp;  
    out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );  
end
```

Always Blocks

- Always blocks can contain more advanced control constructs

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        if ( sel == 2'd0 )
            out = a;
        else if ( sel == 2'd1 )
            out = b;
        else if ( sel == 2'd2 )
            out = c;
        else if ( sel == 2'd3 )
            out = d;
        else
            out = 1'bx;
    end

endmodule
```

```
module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            2'd3 : out = d;
            default : out = 1'bx;
        endcase
    end

endmodule
```

Case Statements

- What happens if the case statement is not complete?

```
module mux3( input  a, b, c
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
        endcase
    end

endmodule
```

If sel = 3, mux will output the previous value. What have we created?

Case Statements

- What happens if the case statement is not complete?

```
module mux3( input  a, b, c
             input [1:0] sel,
             output out );

    reg out;

    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            default : out = 1'bx;
        endcase
    end

endmodule
```

We can prevent creating state
with a default statement

Latches and Flip-flops


```
module latch
(
  input  clk,
  input  d,
  output reg q
);

  always @( clk )
  begin
    if ( clk )
      d = q;
  end
endmodule
```

```
module flipflop
(
  input  clk,
  input  d,
  output q
);


  always @( posedge clk )
  begin
    d = q;
  end
endmodule
```

Edge-triggered
always block

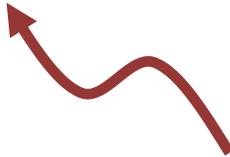

More Verilog Semantics
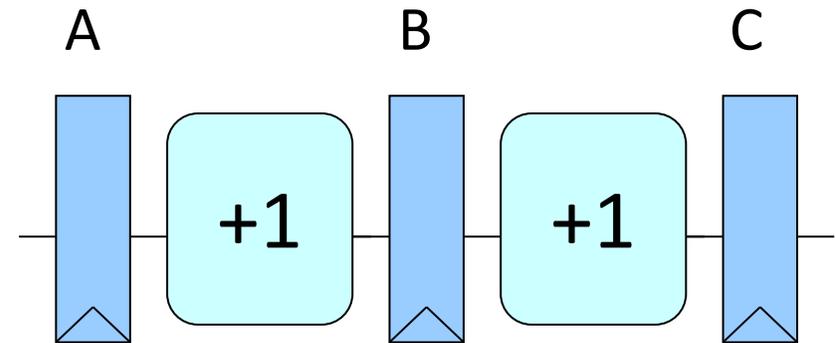
```
wire A_in, B_in, C_in;  
reg  A_out, B_out, C_out;  
  
always @( posedge clk )  
    A_out = A_in;  
  
assign B_in = A_out + 1;  
  
always @( posedge clk )  
    B_out = B_in;  
  
assign C_in = B_out + 1;  
  
always @( posedge clk )  
    C_out = C_in;
```



More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;
    
```

```

always @( posedge clk )
    A_out = A_in;
    
```

```

assign B_in = A_out + 1;
    
```

```


always @( posedge clk )
    B_out = B_in;
    
```

```


assign C_in = B_out + 1;
    
```

```

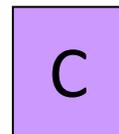always @( posedge clk )
    C_out = C_in;
    
```



Active Event Queue

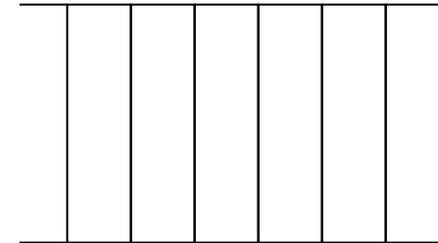

On clock edge all those events which are sensitive to the clock are added to the active event queue in any order!

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;


always @( posedge clk )
    A_out = A_in;

assign B_in = A_out + 1;

always @( posedge clk )
    B_out = B_in;

assign C_in = B_out + 1;

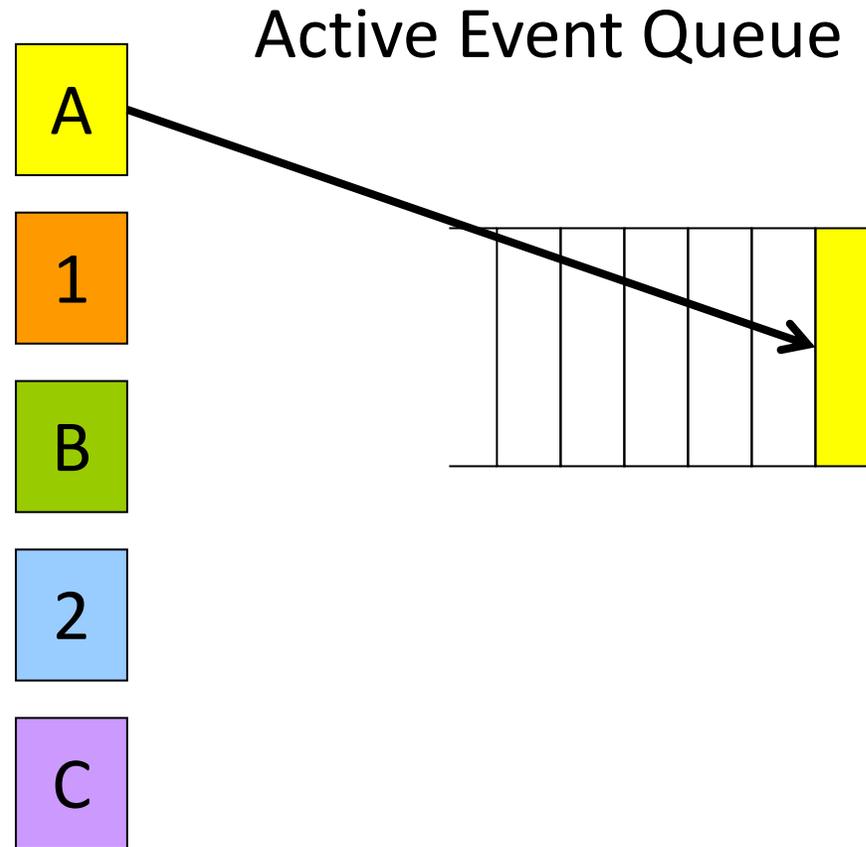always @( posedge clk )
    C_out = C_in;
    
```



More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
    A_out = A_in;


assign B_in = A_out + 1;

always @( posedge clk )
    B_out = B_in;

assign C_in = B_out + 1;

always @( posedge clk )
    C_out = C_in;

```

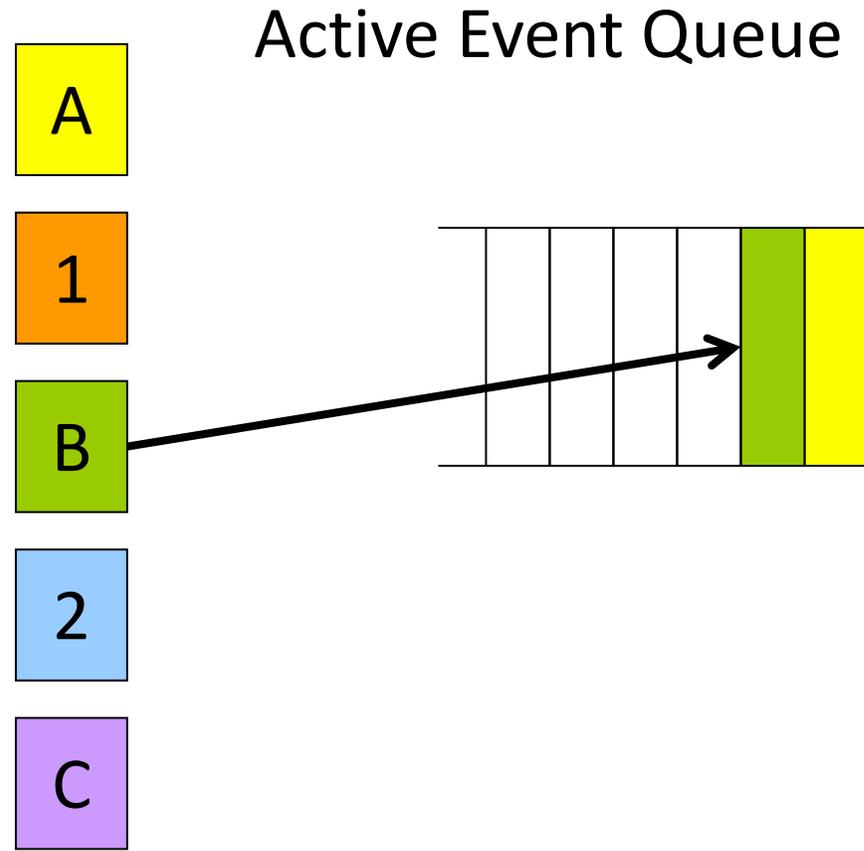

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;


always @( posedge clk )
    A_out = A_in;

assign B_in = A_out + 1;

always @( posedge clk )
    B_out = B_in;

assign C_in = B_out + 1;

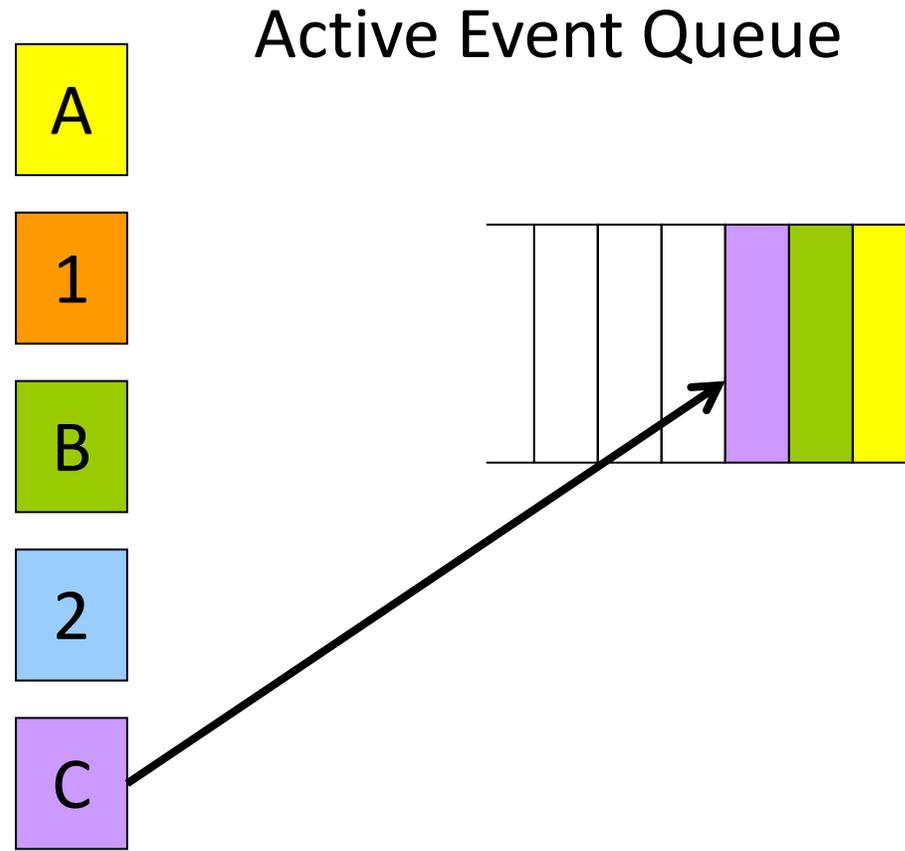always @( posedge clk )
    C_out = C_in;
    
```



More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

```

```

always @( posedge clk )
    A_out = A_in;

```

```

assign B_in = A_out + 1;

```

```

always @( posedge clk )
    B_out = B_in;

```

```


assign C_in = B_out + 1;

```


```

always @( posedge clk )
    C_out = C_in;

```

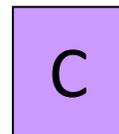

Active Event Queue

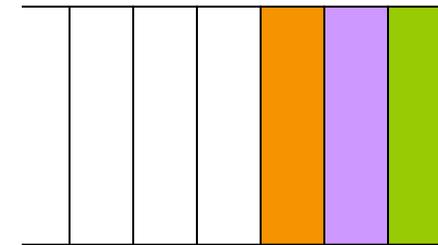

A evaluates and as a consequence 1 is added to the event queue

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

```

```

always @( posedge clk )
    A_out = A_in;

```

```

assign B_in = A_out + 1;

```

```

always @( posedge clk )
    B_out = B_in;

```

```


assign C_in = B_out + 1;

```


```

always @( posedge clk )
    C_out = C_in;

```

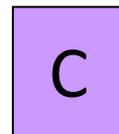

Active Event Queue

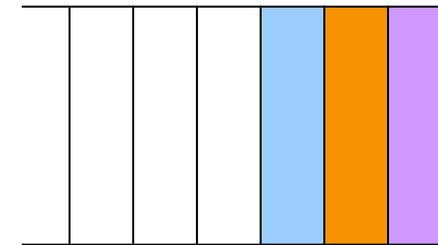

Event queue is emptied
before we go to next clock
cycle

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;
    
```

```

always @( posedge clk )
    A_out = A_in;
    
```

```

assign B_in = A_out + 1;
    
```

```


always @( posedge clk )
    B_out = B_in;
    
```

```


assign C_in = B_out + 1;
    
```

```

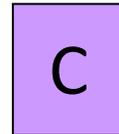always @( posedge clk )
    C_out = C_in;
    
```



Active Event Queue

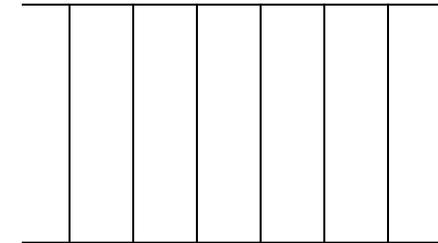

Event queue is emptied
 before we go to next clock
 cycle

More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

```

```

always @( posedge clk )
    A_out = A_in;

```

```

assign B_in = A_out + 1;

```

```

always @( posedge clk )
    B_out = B_in;

```

```




assign C_in = B_out + 1;

```

```

always @( posedge clk )
    C_out = C_in;

```

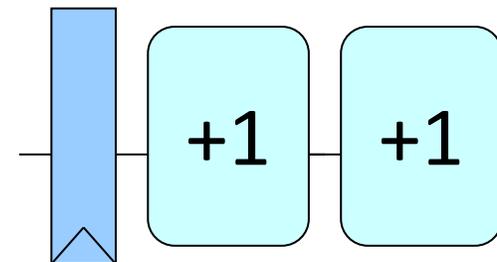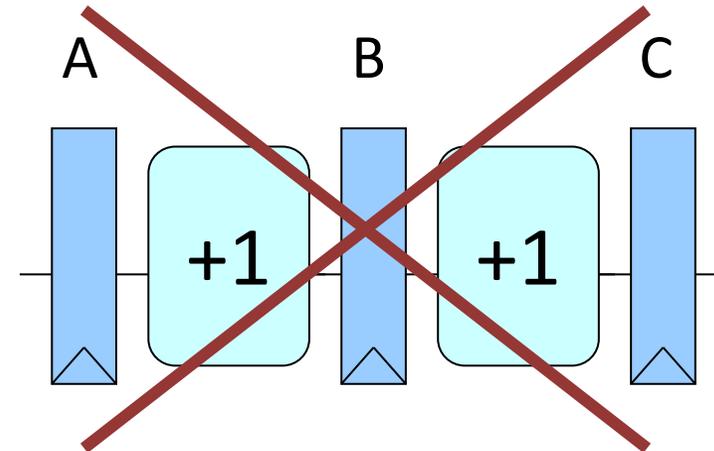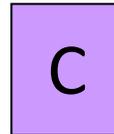

Non-Blocking Assignments

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

```

```

always @( posedge clk )
    A_out <= A_in;

assign B_in = A_out + 1;


always @( posedge clk )
    B_out <= B_in;

assign C_in = B_out + 1;


always @( posedge clk )
    C_out <= C_in;

```

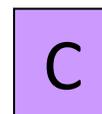
Non-blocking procedural assignments
add an extra event queue



Active Event Queue

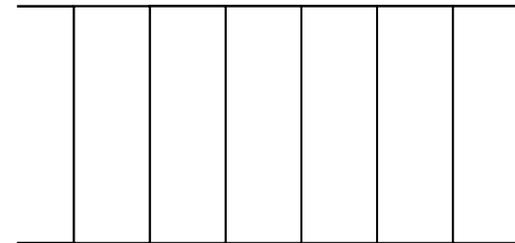

Non-Blocking Queue

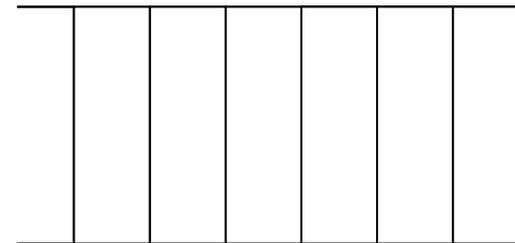

Non-Blocking Assignments

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;
    
```

Non-blocking procedural assignments
 add an extra event queue

```


always @( posedge clk )
    A_out <= A_in;

assign B_in = A_out + 1;

always @( posedge clk )
    B_out <= B_in;

assign C_in = B_out + 1;

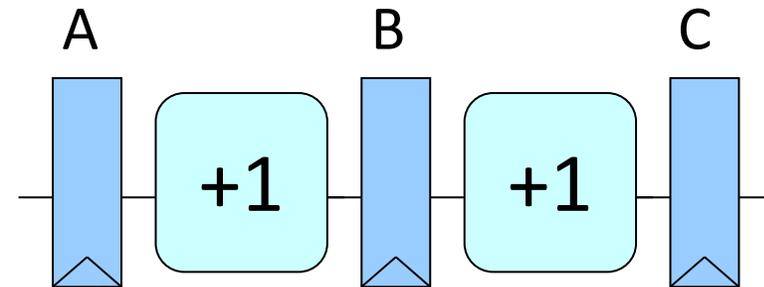always @( posedge clk )
    C_out <= C_in;
    
```



Non-Blocking Assignments

Non-blocking procedural assignments add an extra event queue

```
wire A_in, B_in, C_in;  
reg  A_out, B_out,  
C_out;
```

```
always @(posedge clk )  
begin  
    A_out <= A_in;  
    B_out <= B_in;  
    C_out <= C_in;  
end
```

```
assign B_in = A_out + 1;  
assign C_in = B_out + 1;
```

```
wire A_in, B_in, C_in;  
reg  A_out, B_out,  
C_out;
```

```
always @(posedge clk )  
begin  
    C_out <= C_in;  
    B_out <= B_in;  
    A_out <= A_in;  
end
```


```
assign B_in = A_out + 1;  
assign C_in = B_out + 1;
```

The order of non-blocking assignments does not matter!


Common Patterns

- Common patterns for latch and flip-flop inference

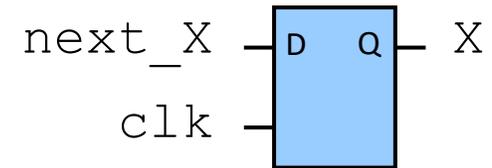
```
always @( clk )
begin
  if ( clk )
    D <= Q;
end
```


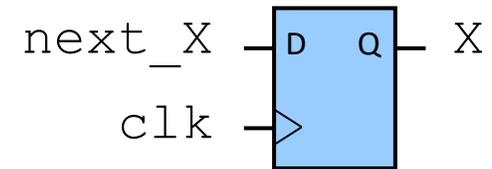
```
always @( posedge clk )
begin
  D <= Q;
end
```


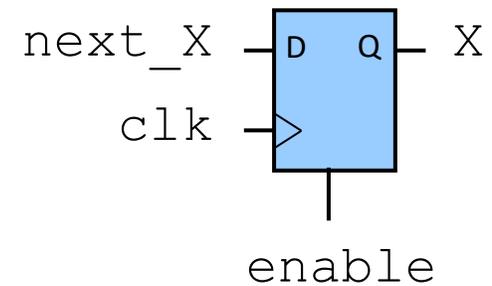
```
always @( posedge clk )
begin
  if ( enable )
    D <= Q;
end
```



Blocking vs. Non-blocking

- Guidelines for using blocking and non-blocking assignment statements
 - Flip-flops should use non-blocking
 - Latches should use non-blocking
 - Combinational logic should use blocking
 - Do not mix combinational and sequential logic in the same always block
 - Do not assign to the same variable from more than one always block

Behavioral Verilog Usage

- Behavioral Verilog is used to model the abstract function of a hardware module
 - Characterized by heavy use of sequential blocking statements in large always blocks
 - Many constructs are not synthesizable but can be useful for behavioral modeling
 - Data dependent for and while loops
 - Additional behavioral datatypes : `integer, real`
 - Magic initialization blocks : `initial`
 - Magic delay statements: `#<delay>`

High-level Behavior

- Verilog can be used to model the high-level behavior of a hardware block

```
module factorial( input [ 7:0] in, output reg  
[15:0] out );
```

```
integer num_calls;  
initial num_calls = 0;
```



Initial statement

```
integer multiplier;  
integer result;
```



Variables of type
integer

```
always @(*)  
begin  
multiplier = in;  
result = 1;  
while ( multiplier > 0 )  
begin  
result = result * multiplier;  
multiplier = multiplier - 1;  
end  
  
out = result;  
num_calls = num_calls + 1;  
end  
endmodule
```



Data dependent
while loop

Delay Statements

- Delay statements should only be used in test

```
module mux4
(
  input      a,
  input      b,
  input      c,
  input      d,
  input [1:0] sel,
  output     out
);
  wire #10 t0 = ~( (sel[1] & c) | (~sel[1] & a) );
  wire #10 t1 = ~( (sel[1] & d) | (~sel[1] & b) );
  wire #10 out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
);

endmodule
```

Although this will add a delay for simulation, these are ignored in synthesis



Synthesizable Blocks


- Even synthesizable blocks can be more behavioral

```
module ALU
(
  input  [31:0] in0,
  input  [31:0] in1,
  input  [ 1:0] fn,
  output [31:0] out
);

  assign out
    = ( fn == 2'd0 ) ? ( in0 + in1 )
    : ( fn == 2'd1 ) ? ( in0 - in1 )
    : ( fn == 2'd9 ) ? ( in1 >> in0 )
    : ( fn == 2'd10 ) ? ( in1 >>> in0 )
    : 32'bx;

endmodule
```

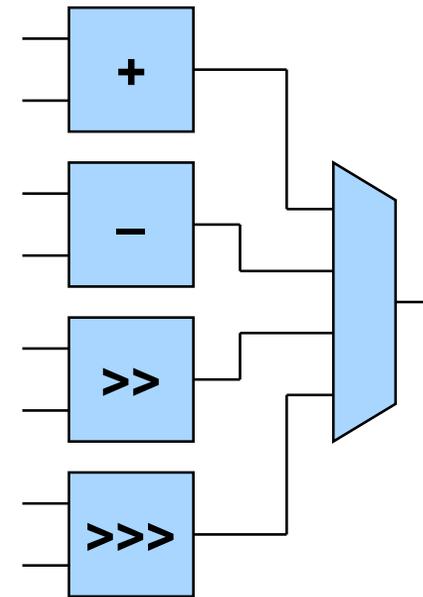Although this module is synthesizable, it is unlikely to produce the desired hardware



System Testing

```
reg [ 1023:0 ] exe_filename;

initial
begin


    // This turns on VCD (plus) output
    $vcdpluson(0);

    // This gets the program to load into memory from the command line
    if ( $value$plusargs( "exe=%s", exe_filename ) )
        $readmemh( exe_filename, mem.m );
    else
    begin
        $display( "ERROR: No executable specified! (use +exe=<filename>)" );
        $finish;
    end

    // Strobe reset
    #0 reset = 1;
    #38 reset = 0;

end
```

Which abstraction is the right one?

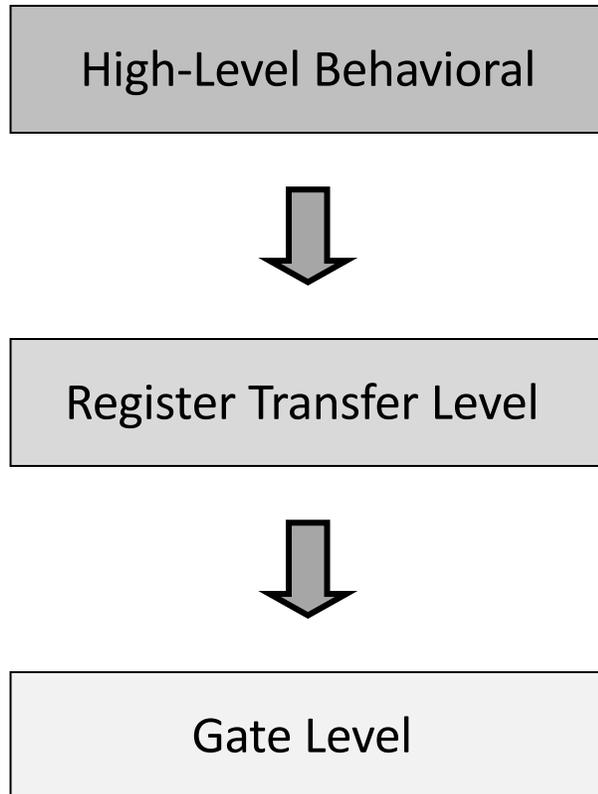

- Designers usually use a mix of all three
 - Early in the design process they might use mostly behavioral models.
 - As the design is refined, the behavioral models begin to be replaced by dataflow models.
 - Finally, the designers use automatic tools to synthesize a low-level gate-level model

Take away points

- Structural Verilog enables us to describe a hardware schematic textually
- Verilog can model hardware at three levels of abstraction
 - Gate level, register transfer level, and behavioral
- Understanding the Verilog execution semantics is critical for understanding blocking + non-blocking assignments
- Designers must have the hardware they are trying to create in mind when they write their Verilog