

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## CSE/CEN 598

### Hardware Security & Trust

Trusted Digital System Design:  
Verilog Fundamentals I

Prof. Michel A. Kinsy & Mishel Paul

1

---

---

---

---

---

---

---


---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University
 
### Computer System Description

- A system is a set of related components that works as a whole to achieve a goal.
- A system contains:
  - Inputs
  - Behavior
  - Outputs
- Behavior is a function that translates inputs to outputs



2

---

---

---

---

---

---

---


---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University
 
### Integrated Circuit Based Designs

- Complex digital integrated circuits (ICs) are manufactured with the advent of Microelectronics Technology
  - The number of components fitted into a standard size IC represents its integration scale, also called density



3

---

---

---

---

---

---

---

---

### Digital System Design

- Characteristics of digital systems
  - Synchronous vs. Asynchronous
  - Sequential vs. Combinational
  - Design parameters

4

---

---

---

---

---

---

---

---

### Digital Design Flow

Design Stage Tools	
HDL Design (Verilog, VHDL, Bluespec)	Text Editor Emacs, Notepad, VI
Verification	Mentor - ModelSim SE Synopsys - Leda
Synthesis	Synopsys - Design Compiler
Test Insertion	Synopsys - TetraMax Mentor - Ictacon
Static Timing Anal.	Synopsys - PrimeTime
Place & Route	Cadence - Senceable/ SOC Encounter Synopsys - Apollo
Clock Tree Insertion	Cadence - Cltgen
Timing Extraction	Synopsys - StarRC Cadence - Pcell
DRC/ANT Checking	Cadence - Assura, Dracula Mentor - Calibre
LVS	Cadence - Assura, Dracula Mentor - Calibre

5

---

---

---

---

---

---

---

---

### Digital Design Flow: FPGA Design

- FPGA-based design as a sub-domain of digital design

6

---

---

---

---

---

---

---

---

STAM Center

SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

ASU Engineering

Arizona State University

RTL Design Tools

- In this class, we will learn the principles of RTL (register level transfer) coding for synthesis tools through the Verilog hardware description language (HDL) for the design and documentation of out electronic systems.
  - Verilog allows designers to design at various levels of abstraction.
  - It is the most widely used HDL

7

---

---

---

---

---

---

---

---

STAM Center

SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

ASU Engineering

Arizona State University

Programmable Logics

- Field Programmable Gate Arrays (more on it later)
  - Each cell in array contains a programmable logic function

The diagram illustrates the architecture of a Field Programmable Gate Array (FPGA). It features a grid of logic blocks (represented by orange squares) and I/O blocks (represented by blue squares). The logic blocks are interconnected by a network of interconnects (represented by grey lines). Labels with arrows point to a 'Logic Block', an 'I/O Block', and an 'Interconnect'.

8

---

---

---

---

---

---

---

---

STAM Center

SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

ASU Engineering

Arizona State University

Programmable Logics

- Field Programmable Gate Arrays (more on it later)
  - Array has programmable interconnect between logic functions

This diagram provides a detailed view of the internal architecture of an FPGA. It shows a grid of logic blocks, each containing a Look-Up Table (LUT) and a flip-flop. The logic blocks are interconnected by a network of routing wires. Other components shown include three-state buffers, configuration memory, and a multiplexer (Mux). Labels with arrows identify these various components.

9

---

---

---

---

---

---

---

---

## Verilog Fundamentals

- Data types
- Structural Verilog
- Functional Verilog
  - Gate level
  - Register transfer level
  - High-level behavioral

10

---

---

---

---

---

---

---

## Primary Verilog data type

- Primary Verilog data type is a bit-vector where bits can take

Value	Meaning
0	Logic zero
1	Logic one
X	Unknown logic value
Z	High impedance, floating

An X bit might be a 0, 1, Z, or in transition. We can set bits to be X in situations where we don't care what the value is. This can help catch bugs and improve synthesis quality

11

---

---

---

---

---

---

---

## Verilog wire

- The Verilog keyword `wire` is used to denote a standard hardware net

```

wire [15:0] instruction;
wire [15:0] memory_req;
wire [ 7:0] small_net;

```

Absolutely no type safety when connecting nets!

12

---

---

---

---

---

---

---

**Verilog bit literals**

- Verilog includes ways to specify **bit literals** in various bases

4' b10\_11

↑      ↑      ↑

Base format (d,b,o,h)

Decimal number representing size in bits

Underscores are ignored

- Binary literals
  - 8'b0000\_0000
  - 8'b0xx0\_1xx1
- Hexadecimal literals
  - 32'h0a34\_def1
  - 16'haxxx
- Decimal literals
  - 32'd42

13

---

---

---

---

---

---

---

---

**Verilog module specification**

- A Verilog module includes a module name and a port list

Ports must have a direction (or be bidirectional) and a bitwidth

```

module adder( A, B, cout, sum );
input  [3:0] A;
input  [3:0] B;
output  cout;
output [3:0] sum;

// HDL modeling of
// adder functionality

endmodule

```

Note the semicolon at the end of the port list!

14

---

---

---

---

---

---

---

---

**Verilog module specification**

- A Verilog module includes a module name and a port list

**Traditional Verilog-1995 Syntax**

```

module adder( A, B, cout, sum );
input  [3:0] A;
input  [3:0] B;
output  cout;
output [3:0] sum;

```

**ANSI C Style Verilog-2001 Syntax**

```

module adder( input  [3:0] A,
              input  [3:0] B,
              output  cout,
              output [3:0] sum );

```

15

---

---

---

---

---

---

---

---

### Module composition

- A module can instantiate other modules creating a module

```

module FA( input a, b, cin
          output cout, sum
);
    // HDL modeling of 1 bit
    // adder functionality
endmodule

```

16

---

---

---

---

---

---

---

---

### Module composition

```

module adder( input [3:0] A, B,
              output cout,
              output [3:0] S );

    wire c0, c1, c2;
    FA fa0( ... );
    FA fa1( ... );
    FA fa2( ... );
    FA fa3( ... );
endmodule

```

17

---

---

---

---

---

---

---

---

### Module composition

```

module adder( input [3:0] A, B,
              output cout,
              output [3:0] S );

    wire c0, c1, c2;
    FA fa0( A[0], B[0], 1'b0, c0, S[0] );
    FA fa1( A[1], B[1], c0, c1, S[1] );
    FA fa2( A[2], B[2], c1, c2, S[2] );
    FA fa3( A[3], B[3], c2, cout, S[3] );
endmodule

```

Carry Chain

18

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## Module composition

- Verilog supports connecting ports by position and by name

**Connecting ports by ordered list**

```
FA fa0( A[0], B[0], 1'b0, c0, S[0] );
```

**Connecting ports by name (compact)**

```
FA fa0( .a(A[0]), .b(B[0]),  
        .cin(1'b0), .cout(c0), .sum(S[0]) );
```

**Connecting ports by name**

```
FA fa0  
(  
    .a    (A[0]),  
    .b    (B[0]),  
    .cin   (1'b0),  
    .cout  (c0),  
    .sum   (S[0])  
);
```

For all but the smallest modules,  
connecting ports by name yields clearer  
and less buggy code.

19

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## Functional Verilog

- Functional Verilog can roughly be divided into three abstraction levels

**Behavioral Algorithm**

Manual

**Abstract algorithmic description**

**Register Transfer Level**

Logic Synthesis

**Describes how data flows between state elements for each cycle**

**Gate Level**

Auto Place + Route

**Low-level netlist of primitive gates**

20

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## Gate-level Verilog

```
module mux4( input  a, b, c, d, input [1:0] sel, output out );  
    wire [1:0] sel_b;  
    not not0( sel_b[0], sel[0] );  
    not not1( sel_b[1], sel[1] );  
    wire n0, n1, n2, n3;  
    and and0( n0, c, sel[1] );  
    and and1( n1, a, sel_b[1] );  
    and and2( n2, d, sel[1] );  
    and and3( n3, b, sel_b[1] );  
    wire x0, x1;  
    nor nor0( x0, n0, n1 );  
    nor nor1( x1, n2, n3 );  
    wire y0, y1;  
    or or0( y0, x0, sel[0] );  
    or or1( y1, x1, sel_b[0] );  
    nand nand0( out, y0, y1 );  
endmodule
```

21

---

---

---


---

---


---

---

---



STAM Center  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS



ASU Engineering  
Arizona State University

## Continuous Assignments

- Continuous assignment statements assign one net to another or to a literal

**Explicit continuous assignment**

```
wire [15:0] netA;
wire [15:0] netB;

assign netA = 16'h3333;
assign netB = netA;
```

**Implicit continuous assignment**

```
wire [15:0] netA = 16'h3333;
wire [15:0] netB = netA;
```

22

---

---

---


---

---


---

---

---



STAM Center  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS



ASU Engineering  
Arizona State University

## Continuous Assignments

- Using continuous assignments to implement an RTL four input multiplexer

```
module mux4( input  a, b, c, d
            input [1:0] sel,
            output out );

    wire out, t0, t1;

    assign t0 = ~( (sel[1] & c) | (~sel[1] & a) );
    assign t1 = ~( (sel[1] & d) | (~sel[1] & b) );
    assign out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );

endmodule
```

The order of these continuous assignment statements does not matter. They essentially happen in parallel!

23

---

---

---


---

---


---

---

---



STAM Center  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS



ASU Engineering  
Arizona State University

## Other Verilog Operators

- Verilog RTL includes many operators in addition to basic boolean logic

```
// Four input multiplexer
module mux4( input  a, b, c, d
            input [1:0] sel,
            output out );

    assign out = ( sel == 0 ) ? a :
                ( sel == 1 ) ? b :
                ( sel == 2 ) ? c :
                ( sel == 3 ) ? d : 1'bx;

endmodule
```

If input is undefined, we want to propagate that information

```
// Simple four bit adder
module adder( input  [3:0] op1, op2,
            output [3:0] sum );

    assign sum = op1 + op2;

endmodule
```

24

---

---

---

---

---

---

---

---



STAM Center

SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

ASU Engineering

Arizona State University

### Verilog RTL operators

Arithmetic	+ - * / % **	Reduction	& ~&   ~  ^ ^~
Logical	! &&	Shift	>> << >>> <<<
Relational	> < >= <=	Concatenation	{ }
Equality	== != === !==	Conditional	?:
Bitwise	~ &   ^ ^~		

```

wire [ 3:0] net1 = 4'b00xx;
wire [ 3:0] net2 = 4'b1110;
wire [11:0] net3 = { 4'b0, net1, net2 };
wire equal = ( net3 == 12'b0000_1110_00xx );

```

Avoid (/ % \*\*) since the usually synthesize poorly

25

---

---

---

---

---

---

---

---

STAM Center

SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

ASU Engineering

Arizona State University

### Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
            input [1:0] sel,
            output out );
    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( sel[1] & c ) | (~sel[1] & a );
        t1 = ~( sel[1] & d ) | (~sel[1] & b );
        out = ~( t0 | sel[0] ) & ( t1 | ~sel[0] );
    end
endmodule

```

The always block is reevaluated whenever a signal in its sensitivity list changes

26

---

---

---

---

---

---

---

---

STAM Center

SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

ASU Engineering

Arizona State University

### Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
            input [1:0] sel,
            output out );
    reg out, t0, t1;

    always @( a or b or c or d or sel )
    begin
        t0 = ~( sel[1] & c ) | (~sel[1] & a );
        t1 = ~( sel[1] & d ) | (~sel[1] & b );
        out = ~( t0 | sel[0] ) & ( t1 | ~sel[0] );
    end
endmodule

```

The order of these procedural assignment statements does matter.  
They essentially happen in sequentially!

27

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
  reg out, t0, t1;

  always @( a or b or c or d or sel )
  begin
    t0 = ~( sel[1] & c ) | ( ~sel[1] & a );
    t1 = ~( sel[1] & d ) | ( ~sel[1] & b );
    out = ~( t0 | sel[0] ) & ( t1 | ~sel[0] );
  end
endmodule

```

LHS of procedural assignments must be declared as a reg type. Verilog reg is not necessarily a hardware register!

28

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
  reg out, t0, t1;

  always @( a or b or c or or sel )
  begin
    t0 = ~( sel[1] & c ) | ( ~sel[1] & a );
    t1 = ~( sel[1] & d ) | ( ~sel[1] & b );
    out = ~( t0 | sel[0] ) & ( t1 | ~sel[0] );
  end
endmodule

```

What happens if we accidentally forget a signal on the sensitivity list?

29

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### Procedural Assignments

- Always blocks have parallel inter-block and sequential intra-block semantics

```

module mux4( input  a, b, c, d
             input [1:0] sel,
             output out );
  reg out, t0, t1;

  always @( a or b or c or d or sel )
  begin
    t0 = ~( sel[1] & c ) | ( ~sel[1] & a );
    t1 = ~( sel[1] & d ) | ( ~sel[1] & b );
    out = ~( t0 | sel[0] ) & ( t1 | ~sel[0] );
  end
endmodule

```

Verilog-2001 provides special syntax to automatically create a sensitivity list for all signals read in the always block

30

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## Assignments

- Continuous and procedural assignment statements are very different

Continuous assignments are for naming and thus we cannot have multiple assignments for the same wire

```

wire out, t0, t1;
assign t0 = ~(sel[1] & c) | (~sel[1] & a);
assign t1 = ~(sel[1] & d) | (~sel[1] & b);
assign out = ~(t0 | sel[0]) & (t1 | ~sel[0]);

```

Procedural assignments hold a value semantically, but it is important to distinguish this from hardware state

```

reg out, t0, t1, temp;
always @( * )
begin
    temp = ~(sel[1] & c) | (~sel[1] & a);
    t0 = temp;
    temp = ~(sel[1] & d) | (~sel[1] & b);
    t1 = temp;
    out = ~(t0 | sel[0]) & (t1 | ~sel[0]);
end

```

31

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## Always Blocks

- Always blocks can contain more advanced control constructs

```

module mux4( input a, b, c, d,
             input [1:0] sel,
             output out );

    reg out;
    always @( * )
    begin
        if ( sel == 2'd0 )
            out = a;
        else if ( sel == 2'd1 )
            out = b;
        else if ( sel == 2'd2 )
            out = c;
        else if ( sel == 2'd3 )
            out = d;
        else
            out = 1'bx;
    end
endmodule

```

```

module mux4( input a, b, c, d,
             input [1:0] sel,
             output out );

    reg out;
    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            2'd3 : out = d;
            default : out = 1'bx;
        endcase
    end
endmodule

```

32

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## Case Statements

- What happens if the case statement is not complete?

```

module mux3( input a, b, c,
             input [1:0] sel,
             output out );

    reg out;
    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
        endcase
    end
endmodule

```

If sel = 3, mux will output the previous value. What have we created?

33

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### Case Statements

- What happens if the case statement is not complete?

```

module mux3( input  a, b, c
             input [1:0] sel,
             output out );

    reg out;
    always @( * )
    begin
        case ( sel )
            2'd0 : out = a;
            2'd1 : out = b;
            2'd2 : out = c;
            default : out = 1'bx;
        endcase
    end
endmodule

```

We can prevent creating state  
with a default statement

34

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### Latches and Flip-flops

```

module latch
(
    input clk,
    input d,
    output reg q
);
    always @( clk )
    begin
        if ( clk )
            d = q;
    end
endmodule

```

```

module flipflop
(
    input clk,
    input d,
    output q
);
    always @( posedge clk )
    begin
        d = q;
    end
endmodule

```

Edge-triggered  
always block

35

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
    A_out = A_in;

assign B_in = A_out + 1;

always @( posedge clk )
    B_out = B_in;

assign C_in = B_out + 1;

always @( posedge clk )
    C_out = C_in;

```

36

---

---

---

---

---

---

---

---

### More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;

```

A

1

B

2

C

Active Event Queue

On clock edge all those events which are sensitive to the clock are added to the active event queue in any order!

37

---

---

---

---

---

---

---

---

### More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;

```

A

1

B

2

C

Active Event Queue

38

---

---

---

---

---

---

---

---

### More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
  A_out = A_in;

assign B_in = A_out + 1;

always @(posedge clk)
  B_out = B_in;

assign C_in = B_out + 1;

always @(posedge clk)
  C_out = C_in;

```

A

1

B

2

C

Active Event Queue

39

---

---

---



---

---

---

---

---

### More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
  A_out = A_in;

assign B_in = A_out + 1;

always @( posedge clk )
  B_out = B_in;

assign C_in = B_out + 1;

always @( posedge clk )
  C_out = C_in;
  
```

A


1

B

2

C

Active Event Queue

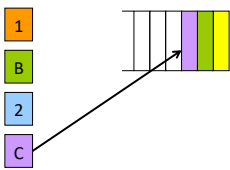

40

---

---

---



---

---

---

---

---

### More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
  A_out = A_in;

assign B_in = A_out + 1;

always @( posedge clk )
  B_out = B_in;

assign C_in = B_out + 1;

always @( posedge clk )
  C_out = C_in;
  
```

A


1

B

2

C

Active Event Queue

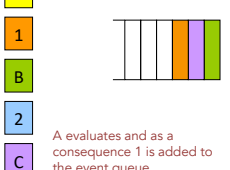

A evaluates and as a consequence 1 is added to the event queue

41

---

---

---



---

---

---

---

---

### More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
  A_out = A_in;

assign B_in = A_out + 1;

always @( posedge clk )
  B_out = B_in;

assign C_in = B_out + 1;

always @( posedge clk )
  C_out = C_in;
  
```

A


1

B

2

C

Active Event Queue

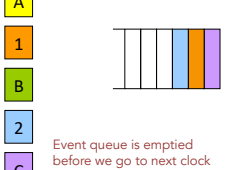

Event queue is emptied before we go to next clock cycle

42

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
  A_out = A_in;

assign B_in = A_out + 1;

always @( posedge clk )
  B_out = B_in;

assign C_in = B_out + 1;

always @( posedge clk )
  C_out = C_in;
  
```

A


1

B

2

C

**Active Event Queue**



Event queue is emptied before we go to next clock cycle

43

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### More Verilog Semantics

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
  A_out = A_in;

assign B_in = A_out + 1;

always @( posedge clk )
  B_out = B_in;

assign C_in = B_out + 1;

always @( posedge clk )
  C_out = C_in;
  
```


A

1

B

2

C

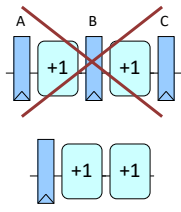

44

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### Non-Blocking Assignments

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @( posedge clk )
  A_out <= A_in;

assign B_in = A_out + 1;

always @( posedge clk )
  B_out <= B_in;

assign C_in = B_out + 1;

always @( posedge clk )
  C_out <= C_in;
  
```

A


1

B


2

C

**Active Event Queue**

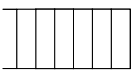

**Non-Blocking Queue**

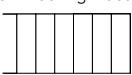

Non-blocking procedural assignments add an extra event queue

45

---

---

---

---

---

---

---

---

**STAM Center** SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

## Non-Blocking Assignments

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
    A_out <= A_in;

assign B_in = A_out + 1;

always @(posedge clk)
    B_out <= B_in;

assign C_in = B_out + 1;

always @(posedge clk)
    C_out <= C_in;

```

Non-blocking procedural assignments add an extra event queue

A

1

B

2

C

46

---

---

---

---

---

---

---

---

**STAM Center** SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

## Non-Blocking Assignments

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
begin
    A_out <= A_in;
    B_out <= B_in;
    C_out <= C_in;
end

assign B_in = A_out + 1;
assign C_in = B_out + 1;

```

```

wire A_in, B_in, C_in;
reg  A_out, B_out, C_out;

always @(posedge clk)
begin
    C_out <= C_in;
    B_out <= B_in;
    A_out <= A_in;
end

assign B_in = A_out + 1;
assign C_in = B_out + 1;

```

Non-blocking procedural assignments add an extra event queue

The order of non-blocking assignments does not matter!

47

---

---

---

---

---

---

---

---

**STAM Center** SECURE, TRUSTED, AND ASSURED MICROELECTRONICS **ASU Engineering** Arizona State University

## Common Patterns

- Common patterns for latch and flip-flop inference

```

always @( clk )
begin
    if ( clk )
        D <= Q;
end

```

→

```

always @(posedge clk)
begin
    D <= Q;
end

```

→

```

always @(posedge clk)
begin
    if ( enable )
        D <= Q;
end

```

→

48

---

---

---

---

---

---

---

---



**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## Blocking vs. Non-blocking

- Guidelines for using blocking and non-blocking assignment statements
  - Flip-flops should use non-blocking
  - Latches should use non-blocking
  - Combinational logic should use blocking
  - Do not mix combinational and sequential logic in the same always block
  - Do not assign to the same variable from more than one always block

49

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## Behavioral Verilog Usage

- Behavioral Verilog is used to model the abstract function of a hardware module
  - Characterized by heavy use of sequential blocking statements in large always blocks
  - Many constructs are not synthesizable but can be useful for behavioral modeling
    - Data dependent for and while loops
    - Additional behavioral datatypes : **integer**, **real**
    - Magic initialization blocks : **initial**
    - Magic delay statements: **#<delay>**

50

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

## High-level Behavior

- Verilog can be used to model the high-level behavior of a hardware block

```

module factorial( input [ 7:0] in, output reg
[15:0] out );
  integer num_calls;
  initial num_calls = 0;
  integer multiplier;
  integer result;

  always @(*)
  begin
    multiplier = in;
    result = 1;
    while ( multiplier > 0 )
    begin
      result = result * multiplier;
      multiplier = multiplier - 1;
    end

    out = result;
    num_calls = num_calls + 1;
  end
endmodule
  
```

Initial statement

Variables of type integer

Data dependent while loop

51

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### Delay Statements

- Delay statements should only be used in test

```

module mux4
(
  input
    a,
  input
    b,
  input
    c,
  input
    d,
  input [1:0] sel,
  output
    out
);
  wire #10 t0 = ~( (sel[1] & c) | (~sel[1] & a) );
  wire #10 t1 = ~( (sel[1] & d) | (~sel[1] & b) );
  wire #10 out = ~( (t0 | sel[0]) & (t1 | ~sel[0]) );
endmodule
  
```

Although this will add a delay for simulation, these are ignored in synthesis

52

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University


### Synthesizable Blocks

- Even synthesizable blocks can be more behavioral

```

module ALU
(
  input [31:0] in0,
  input [31:0] in1,
  input [1:0] fn,
  output [31:0] out
);
  assign out
    = { fn == 2'd0 } ? ( in0 + in1 )
      : { fn == 2'd1 } ? ( in0 - in1 )
      : { fn == 2'd9 } ? ( in1 >> in0 )
      : { fn == 2'd10 } ? ( in1 >>> in0 )
      : 32'bxx;
endmodule
  
```

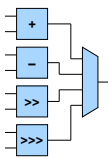Although this module is synthesizable, it is unlikely to produce the desired hardware



53

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### System Testing

```

reg [ 1023:0 ] exe_filename;

initial
begin

  // This turns on VCD (plus) output
  $vcdpluson(0);

  // This gets the program to load into memory from the command line
  if ( $valueplusargs( "exe=", exe_filename ) )
    $readmemh( exe_filename, mem.m );
  else
  begin
    $display( "ERROR: No executable specified! (use -exe=<filename>)" );
    $finish;
  end

  // Strobe reset
  #0 reset = 1;
  #35 reset = 0;

end
  
```

54

---

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### Which abstraction is the right one?

```

graph TD
    A[High-Level Behavioral] --> B[Register Transfer Level]
    B --> C[Gate Level]
  
```

- Designers usually use a mix of all three
  - Early in the design process they might use mostly behavioral models.
  - As the design is refined, the behavioral models begin to be replaced by dataflow models.
  - Finally, the designers use automatic tools to synthesize a low-level gate-level model

55

---

---

---

---

---

---

---

**STAM Center**  
SECURE, TRUSTED, AND ASSURED MICROELECTRONICS

**ASU Engineering**  
Arizona State University

### Take away points

- Structural Verilog enables us to describe a hardware schematic textually
- Verilog can model hardware at three levels of abstraction
  - Gate level, register transfer level, and behavioral
- Understanding the Verilog execution semantics is critical for understanding blocking + non-blocking assignments
- Designers must have the hardware they are trying to create in mind when they write their Verilog

56

---

---

---

---

---

---

---